Name:

**Enrolment No:** 



## UPES End Semester Examination, May 2024 **Course: Electronics** Semester: VIII Time : 03 hrs. **Program: B.Sc. (Chemistry by Research) Course Code: ECEG4046** Max. Marks: 100 Instructions: (i) All questions are compulsory. (ii) Use of Scientific calculator is allowed. SECTION A (5Qx4M=20Marks) S. No. CO Marks An a.c. voltage of peak value of 20V is connected in series with a Si Q1 diode and load resistance of 500 $\Omega$ . If the forward resistance of diode is 5 **CO1** 10 $\Omega$ calculate: (i) peak input voltage, (ii) peak output voltage. For the given circuit; determine $I_c$ and $V_{CB}$ . Q 2 5 **CO2** $2 k\Omega$ VEE Q 3 5 **CO3** $Y = [D + (\overline{A + B}) C]$ Derive and examine the Boolean expression for given circuit. An EM wave is represented by $V = 5(1+0.6\cos 6280 t) \sin 211x10^4 t$ **O**4 volts. What is the maximum and minimum amplitude of wave? What 5 **CO4** frequency components are contained in the modulated wave? **SECTION B** (4Qx10M= 40 Marks) Construct a block diagram of a filter circuit and write its uses? Evaluate Q 5 10 **CO1** the ripple factors for: (i) Choke filter and (ii) Capacitor filter. Q 6 A transistor is connected in common emitter mode as shown in figure. The collector circuit supply is of 8V and the voltage drop across 10 **CO2** resistance Rc is 0.5 V. The value of Rc is given in figure. If $\alpha = 0.96$ determine: (i) collector-emitter voltage and (ii) base-current.

|                                | $I_C$ $I_B$ $V_{CE}$ $R_C = 800 \Omega$ $0.5 V$ $I_E$ $V_{BB}$ $V_{CC} = 8 V$   |    |     |
|--------------------------------|---|----|-----|
| Q 7                            | Illustrate the encoder and decoder circuits with block diagrams.<br>Perform logical operations, by explaining the principle, working and<br>applications of (i) encoders and (ii) decoders. | 10 | CO3 |
| Q 8                            | Derive the mathematical expression for the amplitude modulation of a wave and, hence, define the upper sideband and lower side band frequency.  | 10 | CO4 |
| SECTION-C<br>(20x20M-40 Morta) |   |    |     |
|                                |   |    |     |
| Q 9                            | Calculate the sum of any two and three binary digits for an operation of<br>Binary adders. Illustrate the principle and working of: (i) half and (ii)<br>full adders.                       | 20 | CO3 |
| Q 10                           | What is the phenomenon of modulation? Assume an EM wave and apply the theory of modulation and, hence, estimate modulation-index of the EM wave.  | 20 | CO2 |