
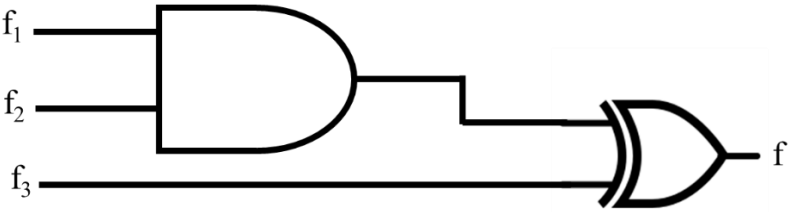
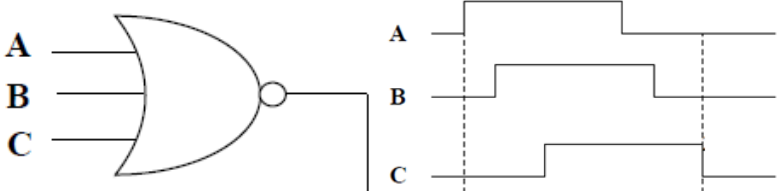


Name:			
Enrolment No:			
UPES End Semester Examination, December 2024			
Course: Digital Electronics Program: BSc Computer Science Course Code: ECEG1010		Semester: I Time: 03 hrs. Max. Marks: 100	
Instructions: Attempt all the questions.			
SECTION A (5Qx4M=20Marks)			
S. No.		Marks	CO
Q 1	<p>Consider three 4-variable functions f_1, f_2 and f_3, which are expressed in sum-of-min terms as $f_1 = \sum(0, 2, 5, 8, 14)$, $f_2 = \sum(2, 3, 6, 8, 14, 15)$, $f_3 = \sum(2, 7, 11, 14)$. For the following circuit with one AND gate and one XOR gate, the output function f can be expressed as?</p> 	4	CO1
Q 2	<p>Convert each of the following binary numbers to octal, decimal, and hexadecimal formats.</p> <p>(a) $(111011101)_2$</p> <p>(b) $(10101010111)_2$</p>	4	CO1
Q 3	<p>Sketch the output waveform for the 3-input NOR gate, showing the proper relation to the input.</p> 	4	CO2
Q 4	Design a full-subtractor using suitable logic gates.	4	CO2
Q 5	Design a 16:1 multiplexer using 4:1 multiplexers.	4	CO3
SECTION B (4Qx10M= 40 Marks)			

Q 6	Simplify the following expressions using K-map (a) $f(W, X, Y, Z) = \sum m(1, 3, 4, 6, 9, 11, 12, 14)$ (b) $f(A, B, C) = \sum m(0, 1, 6, 7) + \sum d(3, 4, 5)$	10	CO1
Q 7	Design a three-bit DOWN Asynchronous counter and draw the output waveforms.	10	CO2
Q 8	Draw the logic circuit of (a) J-K flip-flop using D flip-flop (b) T flip-flop using S-R flip-flop	10	CO3
Q 9	Design a four-bit self-correcting Ring counter using state diagram. OR Design a sequence generator using D flip-flop to generate the sequence 11001011.	10	CO4
SECTION-C (2Qx20M=40 Marks)			
Q 10	What are shift registers? Explain the operation of different types of shift registers along with their circuit diagrams using J-K flip-flops.	20	CO3
Q 11	Design a Mod-12 synchronous UP counter using D flip-flops. OR Design a 3-bit synchronous UP/DOWN counter using J-K flip-flops.	20	CO4