

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, December 2018

Programme Name: B Tech EE, EE-BCT

Course Name : Linear Integrated Circuits

Course Code : ELEG263

Nos. of page(s) : 4

Semester : V


Time : 03 hrs

Max. Marks : 100

Instructions:

- Attempt all questions as per the requirement.
- Assume any data if required and indicate the same clearly. Unless otherwise indicated symbols and notations have their usual meanings.
- Strike off all unused blank pages

SECTION A (20 Marks)

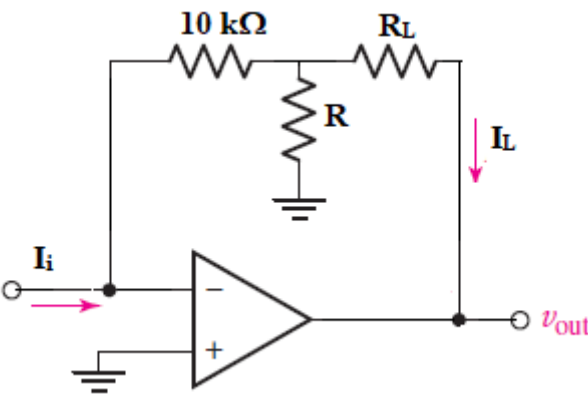S.No.		Marks	CO
Q1	Describe briefly the block diagram of op-amp.	4	CO1
Q2	Assuming the op amp to be ideal, it is required to design the circuit shown in Fig.1 to implement a current amplifier with gain $I_L/I_i=10$. Find the required value for R . 	4	CO2
Q3	What is meant by filter? Give comparison between passive and active filters.	4	CO3
Q4	Write the important features of 555 timer. And also draw the pin diagram of 8-pin DIP 555 timer.	4	CO4
Q5	An 8-bit ADC is capable of accepting an input voltage 0 to 10 V. (a) what is the minimum value of input voltage to cause a digital output change of 1 LSB? (b) What is the digital output code if the applied input voltage is 5.2 V?	4	CO5

SECTION B (40 Marks)

Q6 Consider the noninverting amplifier circuit shown in Fig.2. As shown, the circuit is designed for a nominal gain $1 + \frac{R_2}{R_1}$. It is fed with a low-frequency sine-wave signal of peak voltage V_p and is connected to a load resistor R_L . The op amp is specified to have output saturation voltages of ± 13 V and output current limits of ± 20 mA.

(a) For $V_p = 1$ V and $R_L = 1$ k Ω , calculate v_o, i_L, i_F, i_o for the signal resulting at the output of the amplifier.

(b) For $R_L = 1$ k Ω , what is the maximum value of V_p for which an undistorted sine-wave output is obtained?

(c) For $V_p = 1$ V, what is the lowest value of R_L for which an undistorted sine-wave output is obtained?

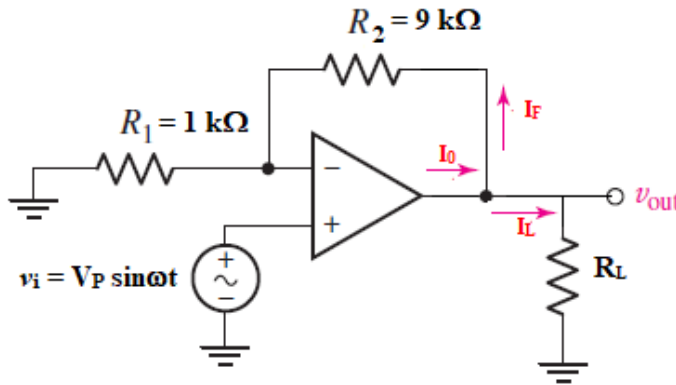


Fig. 2

8

CO1

Q7 A regenerative comparator (Schmitt Trigger) circuit is shown in Fig. 3 (i) Derive expressions for upper threshold and lower threshold voltages, V_{UT} and V_{LT} respectively and hence the value of hysteresis voltage V_H . Calculate V_{UT}, V_{LT}, V_H for the given values of $R_1 = 27$ k Ω and $R_2 = 1$ k Ω . (ii) A sine wave with 2 V peak-to-peak amplitude and 1 kHz frequency is applied at the input of the circuit. Plot the input and output waveforms. $V_{CC} = +15$ V

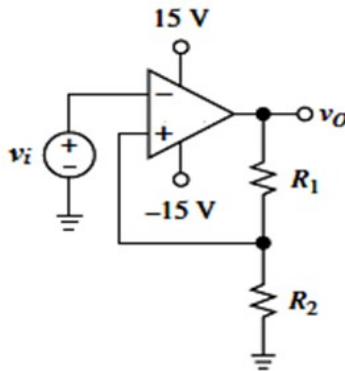
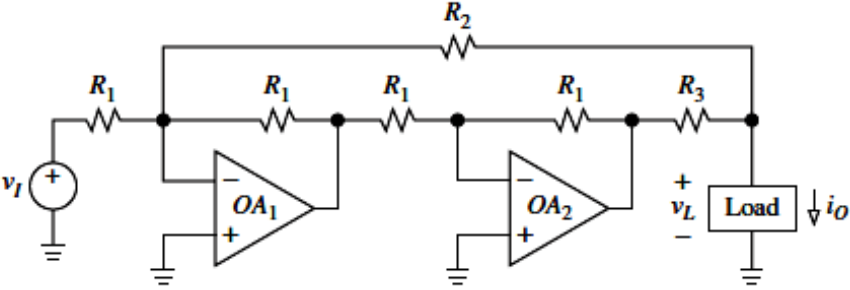


Fig. 3
OR

Draw the generalized circuit diagram of Sallen key second order filter and derive the transfer function of it.

8

CO3

Q8	<p>Draw the block diagrams of the 555 timer Show how 555 can be used as mono-stable multi-vibrator. Describe the circuit operation with the help of waveforms and derive an expression for the frequency of oscillations</p>	8	CO4
Q9	<p>Explain the following op-amp circuits: V-I converter; integrator and differentiator; logarithmic amplifier</p> <p style="text-align: center;">Or</p> <p>Given that the circuit of Fig.4 yields $i_o = A V_i - \frac{V_L}{R_0}$, find the expressions for A and R_0</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Fig. 4</p>	8	CO2
Q10	<p>What are the advantages of R-2R ladder type DAC over weighted binary resistor type? Explain a 4-bit R-2R ladder type DAC in detail.</p>	8	CO5
SECTION-C (40 Marks)			
Q11	<p>(a) To obtain a high-gain, high-input-resistance difference amplifier, the circuit in Fig.5 employs positive feedback, in addition to the negative feedback provided by the resistor R connected from the output to the negative input of the op amp. Specifically, a voltage divider (R_5, R_6) connected across the output feeds a fraction β of the output, that is, a voltage βV_o, back to the positive-input terminal of the op amp through a resistor R. Assume that R_5 and R_6 are much smaller than R so that the current through R is much lower than the current in the voltage divider, with results that $\beta \cong \frac{R_6}{R_5 + R_6}$. Show that the differential gain is given by</p> $A_d = \frac{V_o}{V_{id}} = \frac{1}{1 - \beta}$	10+10	CO2

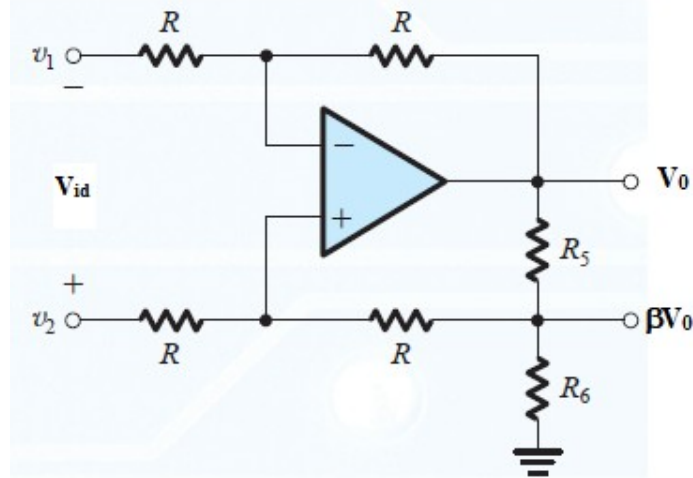


Fig. 5

Design the circuit to obtain a differential gain of 10. Select values for R , R_5 , and R_6 , such that $R_5 + R_6 \leq R/100$

(b) Design an inverting op-amp circuit to form the weighted sum V_0 of two inputs V_1 and V_2 . It is required that $V_0 = -(V_1 + 5V_2)$. Choose values for R_1 , R_2 , and R_F so that for a maximum output voltage of 10 V the current in the feedback resistor will not exceed 1 mA.

Q12

(a) Design an astable multi-vibrator using 555 timer for an oscillating frequency of 10 kHz and a duty cycle of 70%. Assume $C = 0.1 \mu\text{F}$

(b) Design a Multi-feedback second order band pass filter (assume the standard circuit) with bandwidth 10% of center frequency. Given that the center frequency is 10 kHz and $R = 1 \text{ k}\Omega$

OR

The circuit diagram shown in the **Fig.6** is the second order active low pass filter. Determine the transfer function and hence determine the cut-off frequency.

Design this filter with the following parameters: Gain = 20 dB and cut off frequency of 1 kHz; $C_1 = C_2 = 1 \text{ nF}$, $R_1 = R_2 = R_3 = R_4 = R$

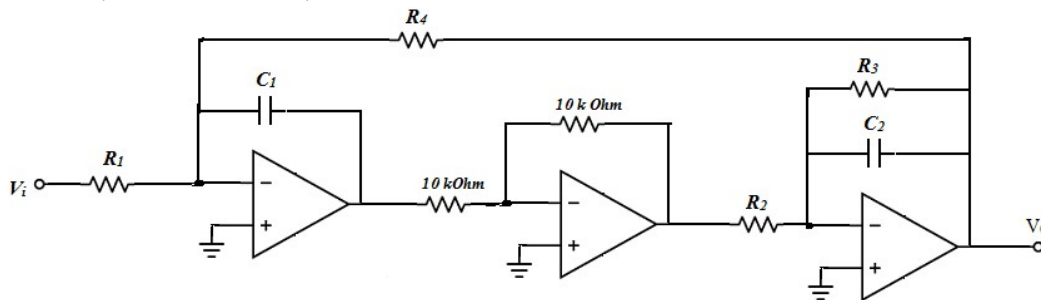


Fig.6

20

CO4

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, December 2018

Programme Name: B Tech EE, EE-BCT

Course Name : Linear Integrated Circuits

Course Code : ELEG263

Nos. of page(s) : 4

Semester : V

Time : 03 hrs

Max. Marks : 100

Instructions:

- Attempt all questions as per the requirement.
- Assume any data if required and indicate the same clearly. Unless otherwise indicated symbols and notations have their usual meanings.
- Strike off all unused blank pages

SECTION A (20 Marks)

S.No.		Marks	CO
Q1	Distinguish between input bias current and input off-set current in op-amp. And then calculate the input bias and off-set currents for an op-amp with input currents $8.3 \mu\text{A}$ and $7.9 \mu\text{A}$.	4	CO1
Q2	Derive the expression of gain for inverting and non-inverting op-amp amplifier.	4	CO2
Q3	Explain the operation of the switched capacitor circuit with necessary circuit diagram and equations	4	CO3
Q4	Define three states in Phased Locked Loop (PLL): free running; capture; phase lock	4	CO4
Q5	A six-bit A/D converter has a maximum precision supply voltage of 20 V. What voltage change does each LSB represent? What voltage does 100110 represent?	4	CO5

SECTION B (40 Marks)

- Q6 In the circuit of **Fig. 1** the pot is used to control gain magnitude as well as polarity. Letting k denote the fraction of R_3 between the wiper and ground, show that varying the wiper from bottom to top varies the gain over the range $-R_2/R_1 \leq \frac{V_0}{V_i} \leq 1$, so that making $R_1 = R_2$ yields $-1 \leq \frac{V_0}{V_i} \leq +1$.

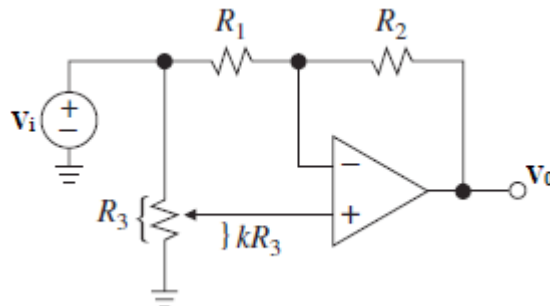
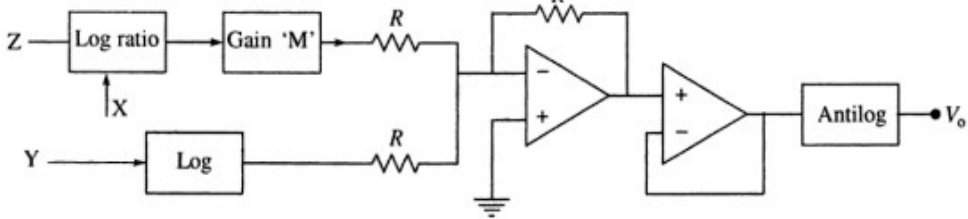
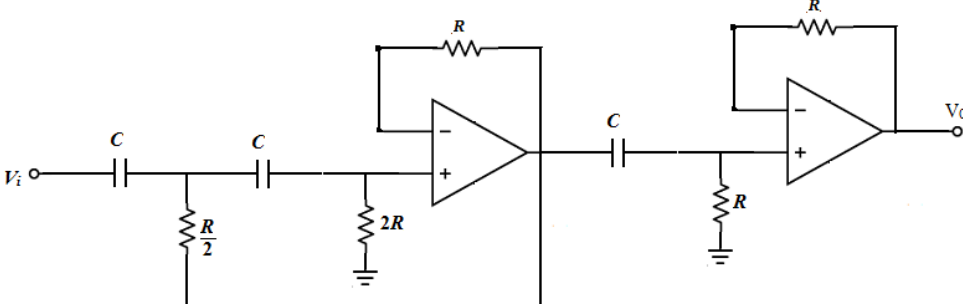


	Fig. 1		
Q7	<p>(a) Explain the following op-amp circuit: sample and hold circuit (b) Determine the output of the circuit shown in Fig.2</p>  <p style="text-align: center;">Fig.2</p>	5+3	CO2
Q8	<p>(a) Sketch and explain operation of the circuit of a 555 timer connected as an astable multi-vibrator. (b) If the frequency of the oscillations of astable multi-vibrator using 555 timer is 350 kHz, determine the value of capacitor C needed using $R_A = R_B = 7.5 \text{ k}\Omega$</p>	6+2	CO4
Q9	<p>Determine the transfer function of 3rd order filter as shown in Fig. 3 and then determine the type of filter (LP, HP, BP or BS filter) and its cut-off frequency. (assume that all op-amp are ideal)</p>  <p style="text-align: center;">Fig. 3</p> <p style="text-align: center;">(Or)</p> <p>Explain the operation of pulse wave form generator using op-amp. Also derive the expression for pulse width of the output signal.</p>	8	CO3
Q10	<p>Describe the operation of dual slope ADC with necessary diagrams. Or Fig. 4 shows a circuit for a digital-to-analog converter (DAC). The circuit accepts a 4-bit input binary word $a_3a_2a_1a_0$, where $a_0, a_1, a_2,$ and a_3 take the values of 0 or 1, and it provides an analog output voltage V_o proportional to the value of the digital input. Each of the bits of the input word controls the correspondingly numbered switch. For instance, if a_2 is 0 then switch S_2 connects the $20 \text{ k}\Omega$ resistor to ground, while if a_2 is 1 then S_2 connects the $20 \text{ k}\Omega$ resistor to the +5 V power supply. Show that V_o is given by</p>	8	CO5

$$V_0 = -\frac{R_f}{10} \frac{V_R}{2^n} (2^3 a_3 + 2^2 a_2 + 2^1 a_1 + 2^0 a_0)$$

Where R_f is in $k\Omega$. Find the value of R_f so that V_0 ranges from 0 to -12 volts.

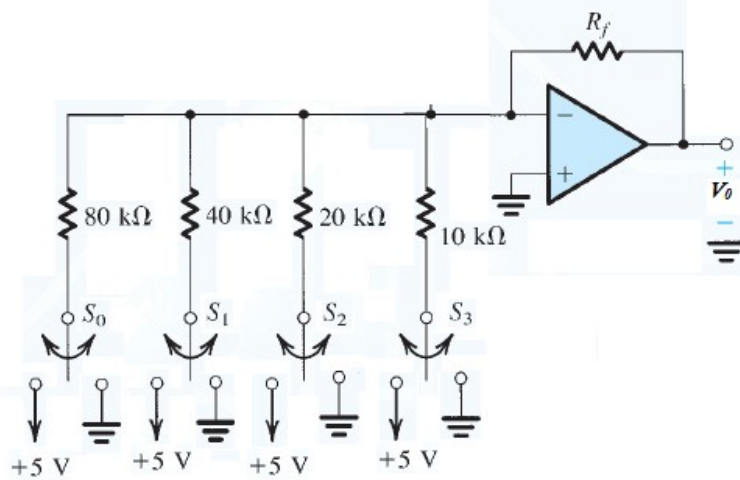


Fig. 4

SECTION-C (40 Marks)

Q11

(a) Design a Saalen key 2nd order high pass filter shown in Fig.5 with a cut-off frequency of 1 kHz, a voltage gain of 20 dB and a quality factor (Q) of 5. Given that $R_1 = R_2 = 1 k\Omega$

10+5+
5

CO3
+CO4
+CO5

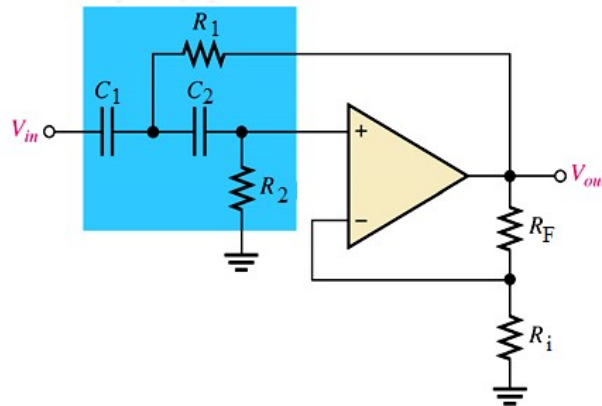


Fig. 5

(b) A PLL IC565 connected as an FM detector has $R_T = 10 k\Omega$, $C_T = 0.01 \mu F$ and $C = 0.04 \mu F$. the supply voltage is +12 V. Determine the free running frequency, lock range and capture range.

(c) Assume you have a 4-bit Successive Approximation type ADC. For the analog input 0.25V; 1.5 and 1.75 V, show how the SAR would approximate the analog input with relevant diagrams. (Given that the V_{ref} is 4V)

Or

The filter circuit of Fig.6 provides the low-pass and band-pass responses using only two op amps. (i) Show that $A_{OBP} = V_{BP}/V_i = -n$, $A_{OLP} = V_{LP}/V_i = m/(m + 1)$, $Q = \sqrt{n(1 + 1/m)}$, and $\omega_0 = Q/nRC$. (ii) Specify component values for a band-pass response with $f_0 = 2$ kHz and $Q = 10$. (iii) What is the resonance gain of your circuit?

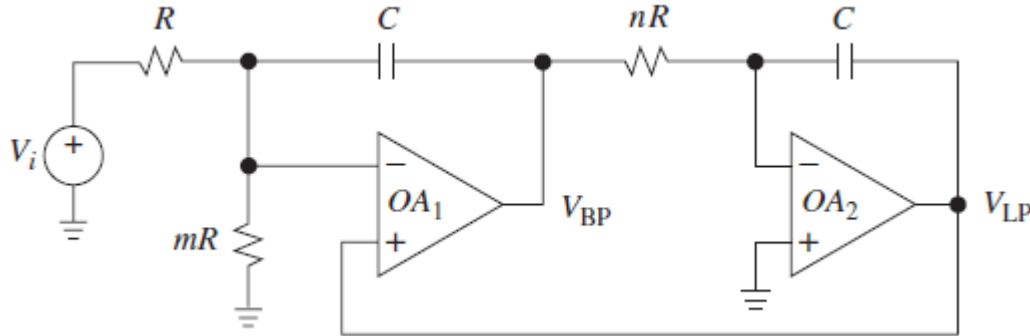


Fig. 6

20

CO3

Q8 (a) Design a circuit depicted in Fig. 7, whose output is $V_O = V_{i1} + 3V_{i2} - 2(V_{i3} + 3V_{i4})$.

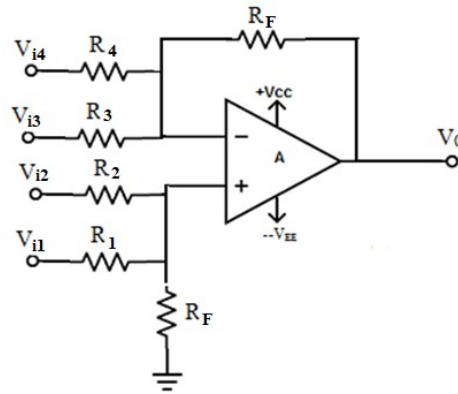


Fig. 7

(b) Design an op-amp circuit to solve the following differential equation

$$A \frac{d^2 V_0}{dt^2} + B \frac{d V_0}{dt} + C V_0 = V_i$$

Where A, B and C are constants. V_0 and V_i are the time dependent voltages.

10+10

CO2