

QUESTION PAPER

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2018

Course: Analog and Digital Electronics (ECEG-2024)
Program: B. Tech- Electrical Engineering
Time: 03 hrs.

Semester: III

Max. Marks: 100

Instructions: Attempt all the sections.

SECTION A (20 Marks)

S. No.	Answer all the questions.	Marks	CO
Q 1	Define a hole in semiconductor and indicate pictorially how it contributes in conduction?	4	CO1
Q 2	Elucidate the two basic processes which are responsible for the movement of electrons and holes in a semiconductor.	4	CO1
Q 3	Determine if the diode (ideal) in Fig. (1) is forward bias or reverse biased.	4	CO2
<p style="text-align: center;">Fig. (1)</p>			
Q 4	Minimize and implement the following multiple output functions using K-map $F_1 = \sum m(1, 2, 3, 6, 8, 12, 14, 15)$ $F_2 = \prod M(0, 4, 9, 10, 11, 14, 15)$	4	CO3
Q 5	Attempt all the parts: (i) $(11011)_2 \rightarrow (?)_{\text{Gray code}}$ (ii) $(10011)_{\text{Gray code}} \rightarrow (?)_2$ (iii) $(126)_{10} \rightarrow (?)_{\text{Excess-3}}$	4	CO3

$$(iv) (1367)_{BCD} \rightarrow (?)_2$$

SECTION B (40 Marks)

Answer all the questions.

Q 6	A binary ripple counter is required to count up to $(16,383)_{10}$. How many FFs are required? If the clock frequency is 8.192MHz, What is frequency at the output of the MSB?	10	CO4
Q 7	<p>Attempt both the parts:</p> <p>(a) How does photo diode differ from an ordinary diode? Analyze the performance characteristics of the photo diode.</p> <p>(b) Derive the expression for the efficiency of a full-wave rectifier.</p>	10	CO2
Q 8	A semiconductor diode having ideal forward and reverse characteristics is used in a half wave rectifier circuit supplying a resistive load of 1000 ohm. If the r.m.s. value is 250V, determine (i) the r.m.s. value of diode current (ii) power dissipated in the load.	10	CO2
Q 9	Determine the operating point of the transistor biasing circuit shown in Fig. (2) by using Thevenin theorem.	10	CO3

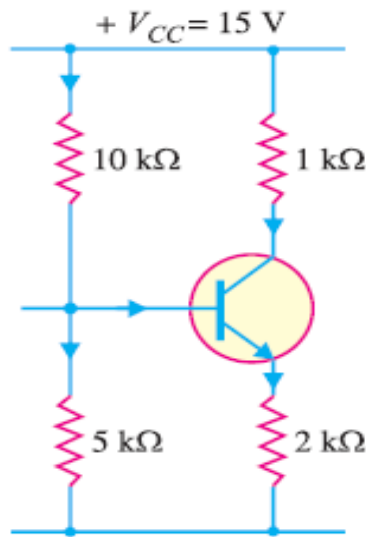


Fig. (2)

OR

Reduce both the Boolean expressions as,

(i)
$$Y = A \left[B + \bar{C} \left(\overline{AB + AC} \right) \right]$$

(ii)
$$Y = (B + BC)(B + \bar{B}C)(B + D)$$

SECTION-C (40 Marks)

Answer all the questions.

Q 10

You are presented with a set of requirements under which an insurance policy can be issued.

The applicant must be:

1. a married female 25 years old or over, or
2. a female under 25, or
3. a married male under 25 who has not been involved in a car accident, or
4. a married male under 25 who has not been involved in a car accident, or
5. a married male 25 years or over who has not been involved in a car accident.

Find an algebraic expression which assumes a value '1' whenever the policy is issued. Simplify the expression obtained and design logic diagram for the same.

15+5

CO3

Q 11

- **Attempt both the parts:**

- a) Design a synchronous BCD counter using J-K flip flops.
- b) Design a logic circuit with 4 inputs A, B, C, D that will produce output '1' only whenever two adjacent input variables are 1s. "A and D are also to be treated as adjacent." Implement it using 'OR' universal logic gate.

OR

Design a circuit that can be built using AOI logic and output is '1' when a 4-bit BCD code translated to a number that uses the upper right segment of a single 7-Segment display system.

10+10

**CO4/
CO3**

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2018


Course: Analog and Digital Electronics (ECEG-2024)
Program: B. Tech- Electrical Engineering
Time: 03 hrs.

Semester: III

Max. Marks: 100

Instructions: Attempt all the sections.

SECTION A (20 Marks)

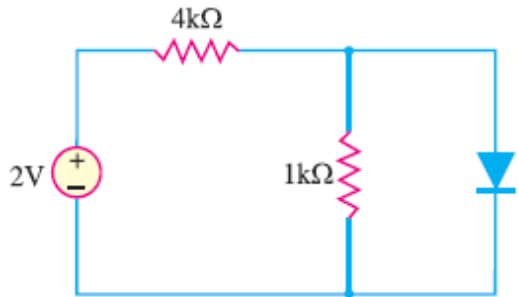S. No.	Answer all the questions.	Marks	CO
Q 1	How does a tunnel diode work and analyze tunneling effect in tunnel diode with the performance characteristics.	4	CO1
Q 2	Determine the state of diode for the circuit shown in Fig. (1) and find I_D and V_D . Assume simplified model for the diode.  Fig. (1)	4	CO2
Q 3	Minimize the following multiple output functions $F_1 = \sum m(0, 2, 6, 10, 11, 12, 13) + d(3, 4, 5, 14, 15)$ $F_2 = \sum m(1, 2, 6, 7, 8, 13, 14, 15) + d(3, 5, 15)$	4	CO3
Q 4	(i) $(123)_{10} \rightarrow (?)_{\text{Excess-3}}$ (ii) $(110110)_2 \rightarrow (?)_{\text{Gray code}}$ (ii) $(11011)_{\text{Gray code}} \rightarrow (?)_2$ (iv) $(1275)_{BCD} \rightarrow (?)_2$	4	CO3
Q 5	How combinational circuits are differing from the sequential circuits? Defend it with the specific reasons.	4	CO4

SECTION B (40 Marks)

	Answer all the questions.		
Q 6	For what minimum value of propagation delay in each flip-flop (FF) will a 10-bit ripple counter skip a count when it is clocked at 10MHz?	10	CO4
Q 7	<p>Attempt the both parts:</p> <p>(a) Derive the expression for the efficiency of a Half-wave rectifier.</p> <p>(b) The four diode used in a bridge rectifier circuit have forward resistance which may be considered constant at 1Ω and infinite reverse resistance. The alternating supply voltage is 240 r.m.s. and load resistance is 480Ω. Calculate: (i) mean load current (ii) power dissipated in each diode.</p>	10	CO2
Q 8	Obtain the minimal expression for $F = \sum m(1, 2, 3, 5, 6, 7, 8, 9, 12, 15)$ using the Quine- McCluskey (Tabulation) method.	10	CO3
Q 9	<p>Design a 2- input 2-output synchronous sequential circuit which produces an output $z=1$, whenever any of the following input sequences 1100, 1010, or 1001 occurs. The circuit resets to its initial state after a 1 output has been generated.</p> <p>OR</p> <p>Design and 4-bit binary data B_4, B_3, B_2, B_1 to Gray code converter.</p>	10	CO4

SECTION-C (40 Marks)

	Answer all the questions.		
Q 10	<p>A lawn-sprinkling system is controlled automatically by certain combinations of the following variables,</p> <p>(i) Season ($S=1$, if summer; 0, otherwise)</p> <p>(ii) Moisture content of soil ($M=1$, if High; 0, if Low)</p> <p>(iii) Outside temperature ($T= 1$, if High; 0, if Low)</p> <p>(iv) Outside humidity ($H= 1$, if High; 0, if Low)</p> <p>The sprinkler is turned on under any of the following circumstances,</p> <p>(1) The moisture content is Low in winter</p> <p>(2) The temperature is High and the moisture content is Low in summer</p> <p>(3) The temperature is High and the humidity is High in summer</p> <p>(4) The temperature is Low and the moisture content is Low in summer</p> <p>(5) The temperature is High and the humidity is low.</p> <p>Use a K-map to find the simplest possible logic expression involving the variables S, M, T and H for turning on the sprinkler system.</p>	20	CO3

Q 11

- **Attempt both the parts:**

(a) Design a pulse generator using indirect logic to produce the following waveforms shown in Fig. (2) as,

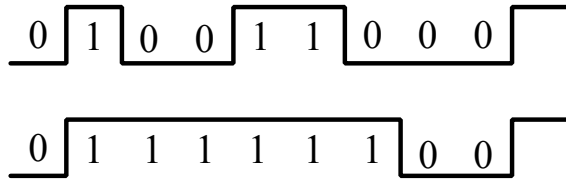


Fig. (2)

(b) Analyze the operation of encoder and design an Octal –to-Binary (8-line to 3-line) encoder.

OR

Design a combinational circuit that accepts a 3-bit BCD number (A, B, D) and generates an output binary number equal to the square of the input numbers.

10+10

CO4/
CO3