

Name:	
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2021

Course: Digital systems and applications Program: BSc (H) Physics Course Code: PHYS 2003	Semester: III Time 03 hrs. Max. Marks: 100
---	---


SECTION A (20 Marks)

1. Each Question will carry 4 Marks
2. Instruction: Attempt all the questions.

S. No.	Question	Marks	COs
Q1	Calculate the speed of electron (mass= 9.1×10^{-31} kg, charge= 1.6×10^{-19} C) after it has moved through a potential difference of 5000 volt in a CRT.	4	CO1
Q2	Convert the $(154)_{10}$ to Binary system, Octal system and Hex system.	4	CO3
Q3	List the various registers of an 8085 microprocessor.	4	CO2
Q4	Define a bus.	4	CO1
Q5	Draw a circuit diagram of a full adder logic circuit with its inputs, outputs and truth table.	4	CO4

SECTION B (40 Marks)

1. Each question will carry 10 marks
2. Instruction: Write short/brief notes (maximum 150 Words).

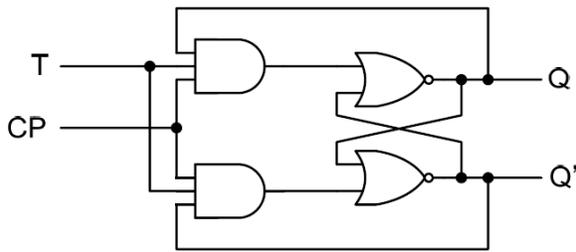Q1	<p>Analyze a given circuit as shown below as an asynchronous sequential circuit. Obtain the transition table and show that the circuit is unstable when both T and CP are equal to 1 (high).</p> <div style="text-align: center; margin: 10px 0;">  </div>	10	CO2
Q2	Digital system in our daily life: At your working place, there is a bell sound to signal quitting time. The bell should be activated when either of the following	10	CO3

	<p>conditions is met:</p> <ol style="list-style-type: none"> 1. it is after 5 o'clock and all employees leave the working place. 2. it is Friday and the work for the day is complete, and all employees left work place. <p>Design a logic circuit that will control the bell sound.</p>		
Q3	A Sensor monitors blood pressure and temperature of your body. Each sensor produces a HIGH voltage when a specified maximum value is exceeded. An alarm requiring a LOW voltage input must be activated when either pressure or temperature is excessive. Design a LOGIC circuit for this application.	10	CO1
Q4	How do you construct a D-flip flop from SR flip-flop? Draw the circuit diagram of a D flip-flop using NAND configuration. Also, make its truth Table.	10	CO2
SECTION-C (40 Marks)			
<p>1. Each Question carries 20 Marks.</p> <p>2. Instruction: Write long answer (maximum 250 Words).</p>			
Q1	What is a microprocessor? Describe any ten main features of 8085 IC.	20	CO2
Q2	What are counters? Differentiate between synchronous and asynchronous counters. Draw a circuit diagram of Ring counter using D-flip flop.	20	CO3