


**UNIVERSITY OF PETROLEUM  
AND ENERGY STUDIES**

**End Semester Examination, May 2018**


|   |                         |
|---|-------------------------|
| <b>Program:</b> B.TECH( ECE, Chem-I&II, ASE,Electrical , PSE, ASE-AVE, APE-Gas-I &II) | <b>Semester – II</b>    |
| <b>Subject (Course):</b> Basic Electrical & Electronics Engineering                   | <b>Max. Marks: 100</b>  |
| <b>Course Code :</b> ECEG1001   | <b>Duration : 3 Hrs</b> |
| <b>No. of page/s:</b> 04  |                         |

---

**Note : All questions are compulsory for Section A and B ,**
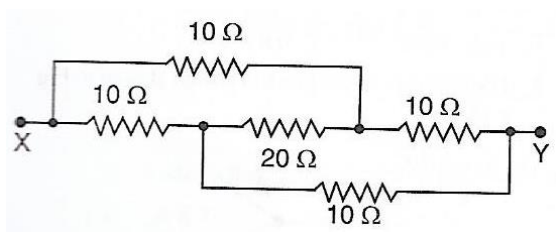
| <b>SECTION A</b> |   |       |                     |
|------------------|---|-------|---------------------|
| 1.               | An electrically driven pump lifts $80 \text{ m}^3$ of water per minute through a height of 12 m . Allowing an overall efficiency of 70 % for the motor and pump , calculate the input power to motor . If the pump is in operation for an average for an average of 2 hours per day for 30 days , calculate the energy consumption in kWh and the cost of energy at the rate of Rs 3.75 per kWh . Assume of $1 \text{ m}^3$ of water has a mass of 1000 kg and $g = 9.81 \text{ m/s}^2$ . | [4]   | <b>CO1</b>          |
| 2.               | A 4 – pole DC Shunt Generator running at 1,500 rpm has an armature with 90 slots having 6 conductors per slot . The flux per pole is $6 \times 10^{-2} \text{ Wb}$ . Determine the induced emf of the DC Generator if the coils are lap connected . If the current per conductor is 100 A , determine the electrical power output of the machine .  | [4]   | <b>CO2</b>          |
| 3.               | Explain all the types of filters used in DC-power supply design with neat sketch  | [4]   | <b>CO3</b>          |
| 4.               | What is the difference between ordinary transformer and Center tapped transformer. Mention the parameters that get changed when using center tapped transformer.  | [4]   | <b>CO3</b>          |
| 5                | (I) Find the equivalent resistance between points X and Y of Fig.1<br><br><div style="text-align: center;">  </div>  | [2+2] | <b>CO1,<br/>CO3</b> |
| <b>Fig.1</b>     |   |       |                     |

|  |   |  |  |
|--|---|--|--|
|  | <p>(II) Find the output voltage and Diode current for the following network shown in Fig 2.</p> |  |  |
|--|---|--|--|

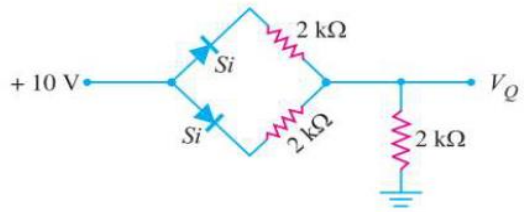


**Fig.2**

|                  |  |  |  |
|------------------|--|--|--|
| <b>SECTION B</b> |  |  |  |
|------------------|--|--|--|

|    |  |            |            |
|----|--|------------|------------|
| 6. | <p>A circuit having a resistance of <math>6 \Omega</math> and inductive reactance of <math>8 \Omega</math> is connected in parallel with another circuit having a resistance of <math>8 \Omega</math> and a capacitive reactance of <math>6 \Omega</math>. The parallel circuit is connected across <math>200 \text{ V}</math>, <math>50 \text{ Hz}</math> supply.</p> <p>Calculate :</p> <p>(i) supply current</p> <p>(ii) power factor of the whole circuit</p> <p>(iii) power consumed .</p> <p>(iv) the resistance and reactance of a series circuit which will take the same current at the same p.f. as the parallel circuit .</p> | <b>[8]</b> | <b>CO1</b> |
|----|--|------------|------------|



|    |  |              |                 |
|----|--|--------------|-----------------|
| 7. | <p>(a) Why is a parallel circuit arrangement best for house wiring?</p> <p>(b) What are the disadvantages of poor power factor in a.c circuit . How we can improve the power factor for any installation/equipment ?</p> | <b>[4+4]</b> | <b>CO1, CO2</b> |
|----|--|--------------|-----------------|

|    |  |            |            |
|----|--|------------|------------|
| 8. | <p>A base current of <math>50 \mu\text{A}</math> is applied to the transistor as shown in figure 3 below and a voltage of <math>5\text{V}</math> is dropped across <math>R_C</math>. Calculate <math>\alpha</math> for the transistor.</p> | <b>[8]</b> | <b>CO3</b> |
|----|--|------------|------------|

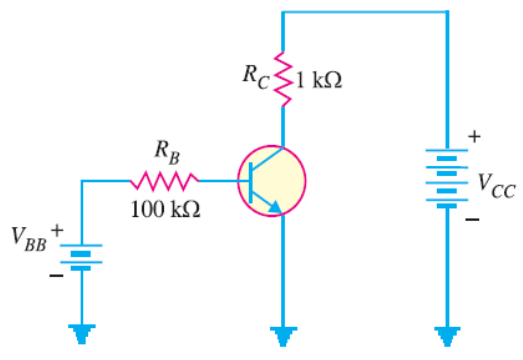

**Fig 3**

|    |   |            |            |
|----|---|------------|------------|
| 9. | <p>Why CE-Amplifier is preferred over CC and CB? Explain working of CB-Configuration Transistor (NPN), draw the input and output characteristics and mention its applications</p> | <b>[8]</b> | <b>CO3</b> |
|----|---|------------|------------|
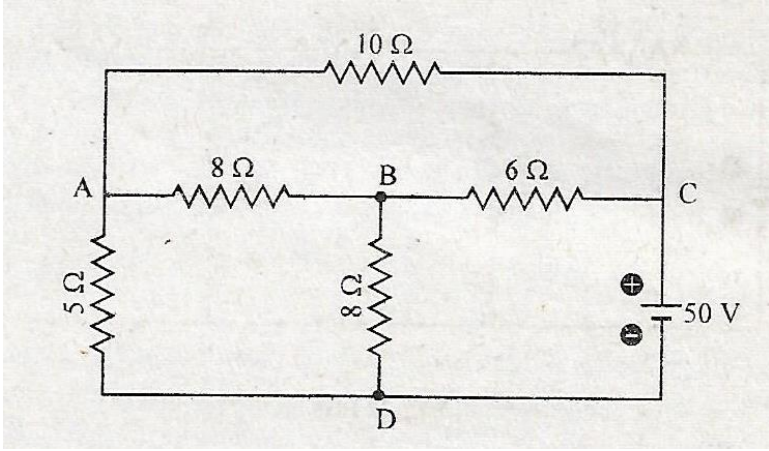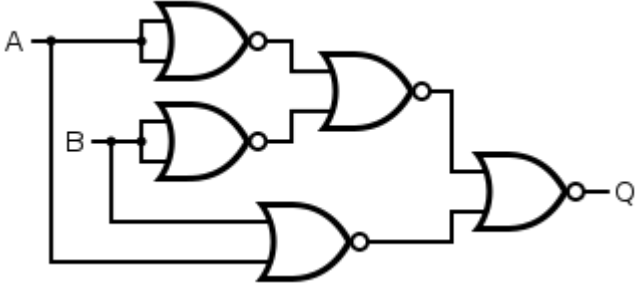
|  |  |               |             |
|--|--|---------------|-------------|
| 10.  | <p>(a) Give the analogy between electric and magnetic circuits . What are the major points of differences between them .</p> <p>(b) For a particular NPN transistor with Emitter bias <math>V_{BE} = 0.7 \text{ V}</math> and <math>\beta = 100</math>, <math>R_B = 430 \text{ K}\Omega</math>, <math>R_C = 2\text{K}\Omega</math>, <math>R_E = 1 \text{ K}\Omega</math>, <math>V_{BB} = 10 \text{ V}</math>, <math>V_{CC} = 20 \text{ V}</math> find <math>I_B</math>, <math>I_C</math> and <math>V_{CE}</math>.</p>  | [4+4]         | CO2,<br>CO3 |
| <b>SECTION C</b><br><b>(Attempt any Two Questions)</b> |  | <b>2 X 20</b> |             |
| 11.  | <p>(a) Using Thevenin's Theorem , determine the current through <math>5 \Omega</math> resistance connected between terminal A and D in the network of Fig 4 below</p> <div style="text-align: center;">  </div> <p style="text-align: center;"><b>Fig 4</b></p> <p>(b) The iron loss of a 80 kVA , 1000/250 V , single phase , 50 Hz transformer is 800 W . The copper loss when primary carries 50 A is 400 W . Estimate :</p> <p>(i) Area of cross – section of limb if working flux density is 1 wb/m<sup>2</sup> and there are 1000 turns on the primary ,</p> <p>(ii) Current ratio ( primary and current)</p> <p>(iii) Efficiency at full load and 0.8 power factor lagging,</p> <p>(iv) Efficiency for a load when copper loss will be equal to iron loss and power factor remains 0.8 lagging</p> | [10,10]       | CO32        |
| 12   | <p>(a) Derive the output equation from the given circuit and implement the same by using logic gates.</p> <div style="text-align: center;">  </div> <p style="text-align: center;"><b>Fig 5</b></p>  | [10,10]       | CO4         |

|     |   |          |          |
|-----|---|----------|----------|
|     | (b) Implement Full adder by using two Half adders and realize the Sum and $C_{out}$ outputs by using NAND gates.  |          |          |
| 13. | <p>(a) Explain with reference to three-phase , the terms ‘Phase sequence’ , and ‘balanced load’ . What will happen if the phase sequence of the supply is changed for 3-phase induction motor .</p> <p>(b) A balanced three-phase star connected load is supplied from a three-phase , 400 V , 50 Hz supply . The resistance of each coil is <math>6 \Omega</math> and reactance is <math>8 \Omega</math> . Find the value of phase current , line current and the total power consumed .</p> <p>(c) Design a Bridge rectifier circuit for which <math>V_{rms}</math> is given as 81.3 V with turn’s ratio 10:1. Find the DC output Voltage <math>V_{DC}</math>, Maximum Value of AC input <math>V_m</math>, Primary &amp; secondary Voltages of Transformer <math>V_1</math> &amp; <math>V_2</math> and Ripple factor. Consider the load resistor to be <math>1K\Omega</math>.</p> | (6+4+10] | CO2, CO4 |

Roll No: -----



**UNIVERSITY OF PETROLEUM  
AND ENERGY STUDIES**

**End Semester Examination, May 2018**

**Program:** B.TECH( ECE, Chem-I&II, ASE,Electrical , PSE, ASE-AVE, APE-Gas-I &II) **Semester – II**  
**Subject (Course):** Basic Electrical & Electronics Engineering **Max. Marks: 100**  
**Course Code :** ECEG1001 **Duration : 3 Hrs**  
**No. of page/s: 04**

---

**Note : All questions are compulsory for Section A and B ,**

| <b>SECTION A</b> |   |         |             |
|------------------|---|---------|-------------|
| 1.               | An electric crane raises a load of 5 tonnes to a height of 30 meters in one minute . Calculate the HP (metric) of the motor and the current taken from a 230 v supply if the efficiency of the crane is 75 % and of the motor is 85 % .   | [4]     | CO1         |
| 2.               | (a) A 3300/300 V single – phase 300 kVA transformer has 1100 primary turns . Find:<br>(i) Transformation ratio<br>(b) secondary turns<br>(c) Voltage/turn<br>(d) Secondary turn when it supplies a load of 200 kW at 0.8 power factor lagging   | [4]     | CO2         |
| 3.               | Explain all the blocks used in DC-Power supply design with neat sketch.   | [4]     | CO3         |
| 4.               | What is the difference between ordinary transformer and Center tapped transformer. Mention the parameters that get changed when using center tapped transformer.  | [4]     |             |
| 5                | (I) Which of the following law/rule can be used to determine the direction of rotation of D.C. motor ?<br>(a) Lenz’s law<br>(b) Fleming’s Right Hand Rule<br>(c) Faradays’s Laws<br>(d) Fleming’s Left Hand Rule<br>(II) The transformer ratings are usually expressed in terms of<br>(a) volts<br>(b) amperes<br>(c) kW<br>(d) kVA<br>(III) Find $I_D$ , $V_D$ and $V_R$ for the following circuit and also determine the value of the Load resistor that results in 10 mA diode current when E is considered as 7V. | [1+1+2] | CO1,<br>2,3 |

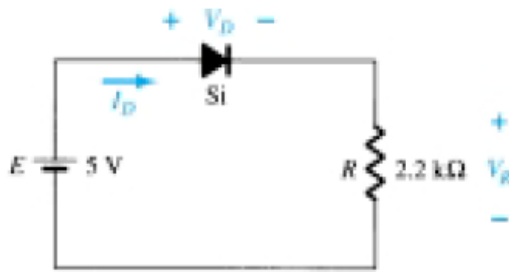


Fig 1

SECTION B

|    |  |       |     |
|----|--|-------|-----|
| 6. | A balanced three – phase load of 3 kW at a power factor of 0.8 lagging is connected across a three – phase supply . If the line current is 12.5 A , calculate the resistance and reactance in each branch of the star connected load . What will be the line current and the power loss if the same load is connected in delta ?   | [8]   | CO1 |
| 7. | (a) Give the limitations of Superposition Theorem .<br><br>(b) A series circuit consisting of resistance $10 \Omega$ , inductive reactance $20 \Omega$ and capacitive reactance $X_c \Omega$ , is connected to 100 V , 50 Hz supply . It is observed that current in the circuit is maximum . Find ,<br>(i) The value of capacitance and inductance in the circuit<br>(ii) The impedance of the circuit<br>(iii) Power factor of the circuit<br>(iv) The value of maximum current .<br>(v) Power consumed by the circuit . | [2,6] | CO1 |
| 8. | A base current of $50 \mu A$ is applied to the transistor as shown in figure 2 and a voltage of 5V is dropped across $R_C$ . Calculate $\alpha$ for the transistor.  | [8]   | CO3 |
| 9. | The BJT amplifier shown in the figure has $h_{fe} = 100$ , $V_{BE} = 0.7V$ . Calculate the value of $R_1$ and $R_C$ such that its $I_C = 1mA$ and $V_{CE} = 2.5 V$   | [8]   | CO3 |

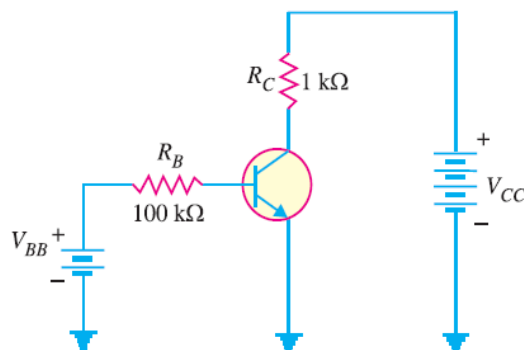


Fig 2

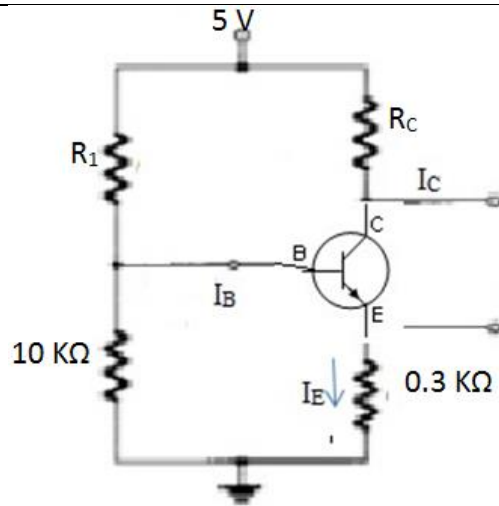


Fig 3

10. (a) Derive an expression for induced e.m.f. in a transformer in terms of frequency, the maximum value of flux and the number of turns on the windings  
 (b) What is PN-junction Diode? Discuss the behavior of a PN junction under forward and reverse biasing and also sketch V-I characteristics of a PN Junction.

[4+4]

CO2

**SECTION C**  
**(Attempt any Two Questions)**

2 X 20

11. (a) A mercury vapour lamp unit consists of a  $25 \mu\text{F}$  condenser in parallel with a series circuit containing the resistive lamp and reactor of negligible resistance. The whole unit takes 400 W at 240 V, 50 Hz and unity power factor. What is the voltage across the lamp?  
 (b) Find the value of adjustable R which results in maximum power transfer across the terminal A – B of the circuit show in Fig 4 below and determine the maximum power.

[10+10]

CO1,  
2

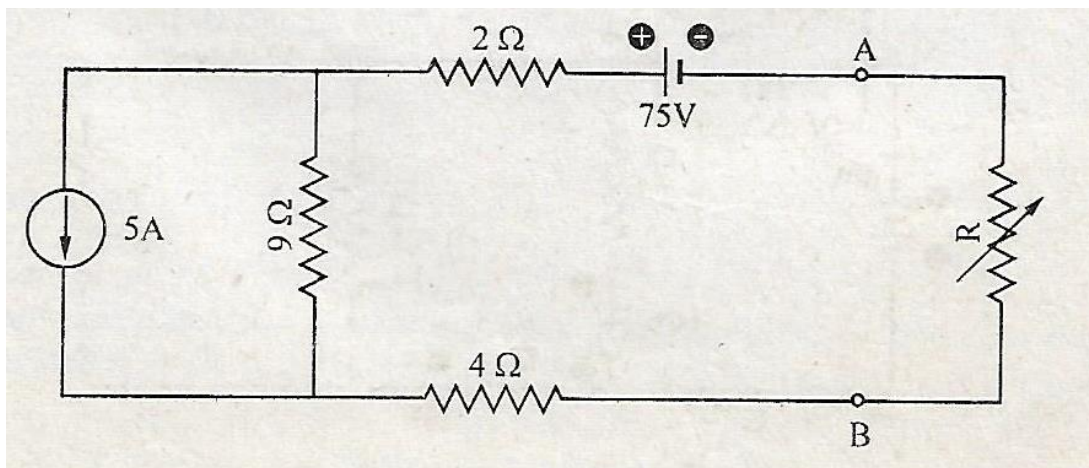


Fig 4

- 12 A) Derive the Boolean equations for F1 and F2, minimize the equations by using Boolean laws and Design the circuit by using logic gates.

CO4

| A | B | C | $F_1$ |
|---|---|---|-------|
| 0 | 0 | 0 | 1     |
| 0 | 0 | 1 | 0     |
| 0 | 1 | 0 | 0     |
| 0 | 1 | 1 | 0     |
| 1 | 0 | 0 | 0     |
| 1 | 0 | 1 | 1     |
| 1 | 1 | 0 | 0     |
| 1 | 1 | 1 | 1     |

| A | B | C | $F_2$ |
|---|---|---|-------|
| 0 | 0 | 0 | 0     |
| 0 | 0 | 1 | 1     |
| 0 | 1 | 0 | 1     |
| 0 | 1 | 1 | 1     |
| 1 | 0 | 0 | 0     |
| 1 | 0 | 1 | 1     |
| 1 | 1 | 0 | 1     |
| 1 | 1 | 1 | 0     |

B) Implement a Full adder by using two Half adders and realize the Sum and  $C_{out}$  outputs by using NAND gates.

13. (a) Explain the principle of operation of dc motors , What is back emf in dc motors ?  
What is its significance ?
- (b) Convert the following
- i.  $(F67.5A)_{16} = ( )_8$
  - ii.  $(101011.1001)_2 = ( )_{10}$
  - iii.  $(9309.124)_{10} = ( )_{16}$
  - iv.  $(101011)_8 = ( )_2$
  - v.  $(679)_8 = ( )_{10}$
- (c). For a particular NPN transistor with Emitter bias  $V_{BE} = 0.7 \text{ V}$  and  $\beta = 200$ ,  $R_B = 50 \text{ K}\Omega$ ,  $R_C = 300 \Omega$ ,  $R_E = 10 \text{ K}\Omega$ ,  $V_{BB} = 10 \text{ V}$ ,  $V_{CC} = 20 \text{ V}$  find  $I_B$ ,  $I_C$  and  $V_{CE}$

**CO2,  
CO4**