

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, April/May 2018

Course: Linear Integrated Circuits (ELEG263)

Semester: IV

Program: B Tech Electrical

Time: 03 hrs.


Max. Marks: 100

No. of page/s: 4

Instructions:

- The question paper contains three sections namely Section-A, Section-B and Section-C.
- Attempt all questions. The number of marks for each question is mentioned on the right side of it.
- Assume any data if required and indicate the same clearly. Unless otherwise indicated symbols and notations have their usual meanings.
- Strike off all unused blank pages

SECTION A (20 Marks)
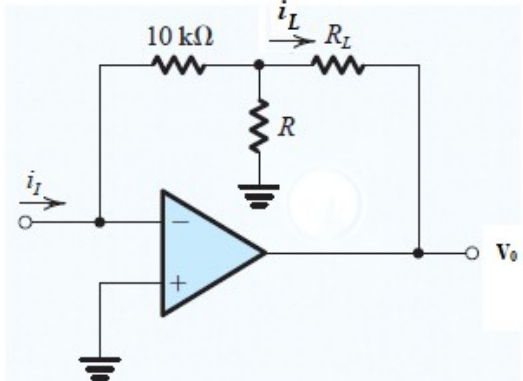
| S. No. | | Marks | CO |
|--------|---|-------|-----|
| Q 1 | <p>(a) The open loop gain of a certain op-amp is 1.75×10^5 and its common mode gain is 0.18. find the CMRR in decibels</p> <p>(b) Distinguish between input bias current and input off-set current in op-amp. And then calculate the input bias and off-set currents for an op-amp with input currents $8.3 \mu\text{A}$ and $7.9 \mu\text{A}$.</p> <p>(c) How long does it take the output voltage of an op-amp to go from -10V to $+10\text{V}$ if the slew rate is $0.5\text{V}/\mu\text{s}$</p> | 1+3+1 | CO1 |
| Q 2 | <p>Assuming the op amp to be ideal, it is required to design the circuit shown in Fig.1 to implement a current amplifier with gain $i_L/i_I=10$. Find the required value for R.</p>  <p>Fig. 1</p> | 5 | CO2 |
| Q 3 | <p>(a) Draw a circuit of 4-bit R-2R ladder DAC using $15\text{ k}\Omega$ and $30\text{ k}\Omega$ resistors.</p> | 5 | CO5 |

| | | | |
|-----|--|---|-----|
| | (b) For a reference voltage of 16 V, calculate the output voltage for an input of 1101 to the above circuit from part (a) | | |
| Q 4 | For the circuit in Fig.2, let the op-amp has saturation voltages be ± 10 V, $R_1 = 100$ k Ω , $R_2 = R = 1$ M Ω , and $C = 0.01$ μ F. Find the frequency of oscillation. | 5 | CO3 |

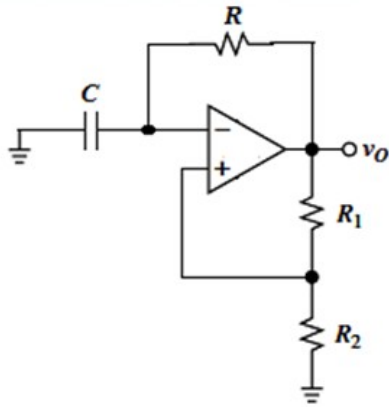


Fig. 2

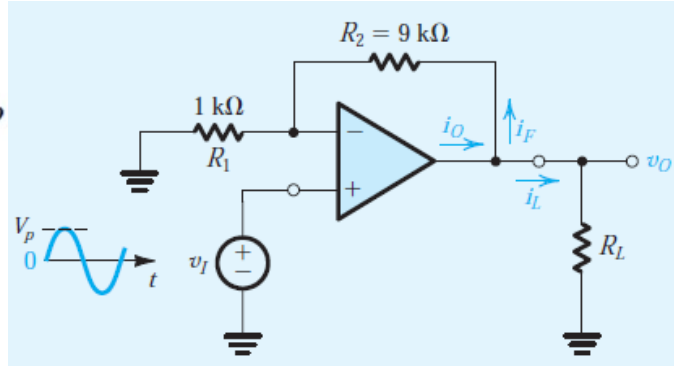


Fig. 3

SECTION B (40 Marks)

| | | | |
|-----|---|-------|-----|
| Q 5 | <p>Consider the noninverting amplifier circuit shown in Fig.3. As shown, the circuit is designed for a nominal gain $1 + \frac{R_2}{R_1}$. It is fed with a low-frequency sine-wave signal of peak voltage V_p and is connected to a load resistor R_L. The op amp is specified to have output saturation voltages of ± 13 V and output current limits of ± 20 mA.</p> <p>(a) For $V_p = 1$ V and $R_L = 1$ kΩ, calculate v_o, i_L, i_F, i_o for the signal resulting at the output of the amplifier.</p> <p>(b) For $R_L = 1$ kΩ, what is the maximum value of V_p for which an undistorted sine-wave output is obtained?</p> <p>(c) For $V_p = 1$ V, what is the lowest value of R_L for which an undistorted sine-wave output is obtained?</p> | 4+2+2 | CO1 |
| Q 6 | <p>(a) Sketch and explain operation of the circuit of a 555 timer connected as an astable multi-vibrator.</p> <p>(b) If the frequency of the oscillations of astable multi-vibrator using 555 timer is 350 kHz, determine the value of capacitor C needed using $R_A = R_B = 7.5$ kΩ.</p> | 6+2 | CO4 |
| Q 7 | With neat block diagram, explain the operation of 8-bit successive approximation register type ADC. What is the maximum conversion time for this type of ADC. | 8 | CO5 |
| Q 8 | Determine the output V_o of the following Op-amp circuit shown in Fig. 4. (Assume that all the Op-amps are ideal). Where $V_1 = 5 + 2\sin\omega t$, $V_2 = 3t + 2\cos\omega t$, $R = 100$ k Ω , $C = 10$ μ F, $R_2 = 2R_1$ | 4+4 | CO2 |

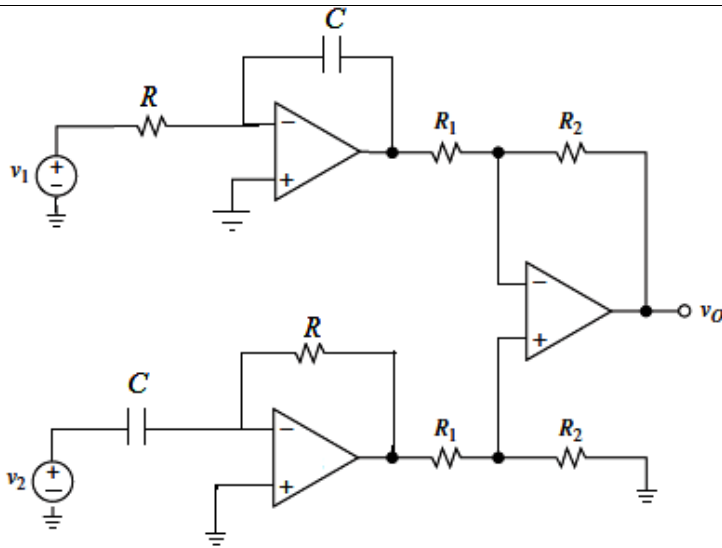


Fig.4

Q9 Determine the transfer function of 3rd order filter as shown in Fig. 5 and then determine the type of filter (LP, HP, BP or BS filter) and its cut-off frequency. (assume that all op-amp are ideal)

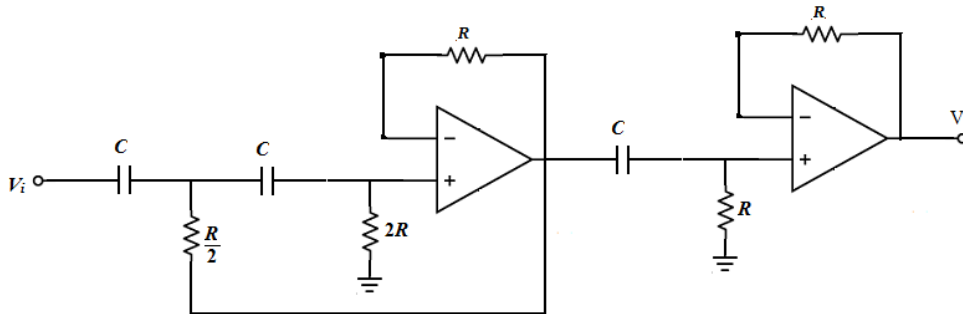


Fig.5

8

CO3

SECTION-C (40 Marks)

Attempt any two questions from this section

Q 10 (a) Design an inverting op-amp circuit to form the weighted sum V_0 of two inputs V_1 and V_2 . It is required that $V_0 = -(V_1 + 5 V_2)$. Choose values for R_1 , R_2 , and R_F so that for a maximum output voltage of 10 V the current in the feedback resistor will not exceed 1 mA.

10+10

CO2

(b) Design the circuit shown in Fig. 6 to have an input resistance of 100 k Ω and a gain V_0/V_i that can be varied from -1 to -10 using the 10 k Ω potentiometer R_4 . What voltage gain results when the potentiometer is set exactly at its middle value?

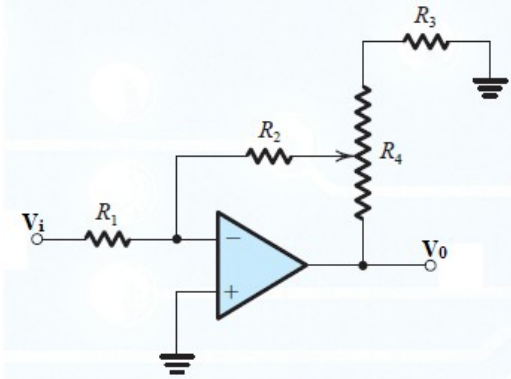


Fig. 6


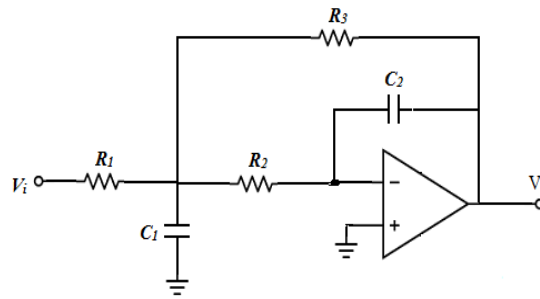


Fig. 7

Q 11 (a) Design a multi-feedback 2nd order low pass filter shown in Fig. 7 with a cut-off frequency of 1 kHz, a voltage gain of 20 dB and a quality factor (Q) of 5. Given that $R_1 = R_2 = 1 \text{ k}\Omega$

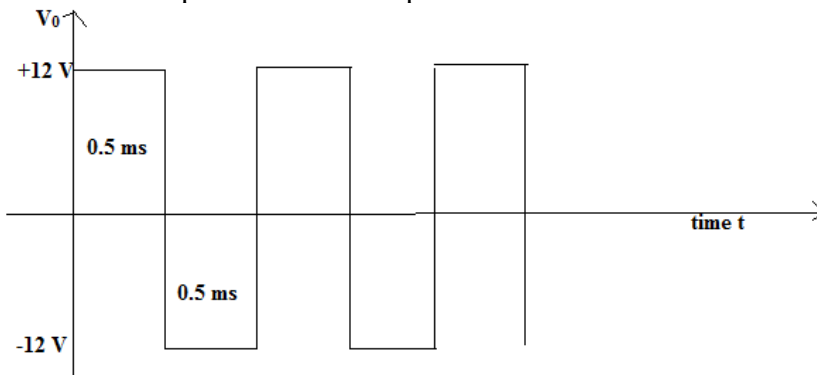(b) Design an op-amp wave form generating circuit to produce the waveform as given below. Explain the circuit operation with relevant waveforms.



10+10

CO3

Q 12 (a) Design an astable multi-vibrator using 555 timer for a frequency of 10 kHz and a duty cycle of 70%. Assume $C = 0.1 \mu\text{F}$

(b) Design a Sallen key second order band pass filter shown in fig. with bandwidth 10% of center frequency. Given that the center frequency is 10 kHz and $R = 1 \text{ k}\Omega$

10+10

CO4