

Name:  
Enrolment No:



**UNIVERSITY OF PETROLEUM AND ENERGY STUDIES**  
**End Semester Examination, December 2018**  
SET-I

**Course:** Automation & Robotics Engineering (ECEG 2014)

**Semester:** I

**Programme:** M.Tech

**Time:** 03 hrs.

**Max. Marks:** 100

**Instructions:**

**SECTION A**

S. No.		Marks	CO
Q 1	Discuss the various filter circuits used for embedded circuits. Also draw the circuit.	4	CO1
Q 2	Discuss in brief the different power supply circuit used to drive a hex- robot	4	CO2
Q 3	Discuss the role of capacitor and freewheeling diode in reducing back EMF from DC motor. Draw the circuit to support your answer.	4	CO2
Q 4	Discuss the rules to design analog and digital circuits in printed circuit boards.	4	CO3
Q 5	Discuss how the cost of processor increases if design is based on increasing speed of a processor. Calculation should base on mathematical expression.	4	CO3

**SECTION B**

Q 6	Design a BJT based amplifier using $\beta_{re}$ model. Calculate the input and output impedances, voltage gain and current gain. Consider the $R_E$ (Emitter resistor) resistor if using self-bias or voltage divider bias based BJT amplifier.	10	CO1
Q 7	List out the aspects for designing the power supply for heavy payload applications with the help of BJT transistors and MOSFET.	10	CO2
Q 8	Design and explain ULN2003 IC and explain the concept of using this driver IC to drive stepper motor.	10	CO3
Q 9	Below is the PCB design of power supply unit of a tiny robot. Comment on the flaws of the design	10	CO3

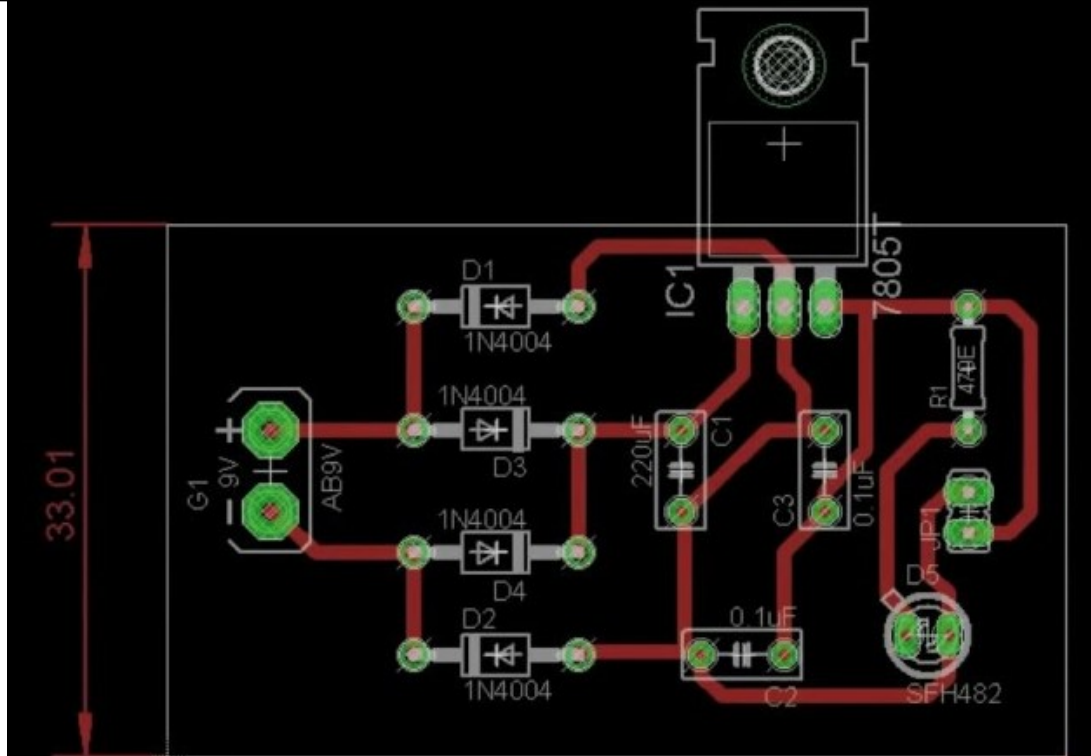


Fig. 1


OR

Q 10	Design a relay based circuit and opto coupler based circuit to drive a robot. List out the advantages and disadvantages using relay and Opto coupler based driver circuits.	10	CO2
------	---	----	-----

SECTION-C

Q 11	Design a white light (from flash light) tracking circuit for a Robot that will track the white light in real time.	20	CO5
------	--	----	-----

Q 12	<p>1. The circuit shows how an 8-bit MUX can be used to generate a four-variable logic function even though the MUX has only 3 SELECT inputs.</p> <p>(a) Setup a truth table showing the output Y for the 16 possible combinations of input variables.</p> <p>(b) Write the sum-of-products expression for Y and simplify it to verify that</p> $Y = \bar{C}B\bar{A} + D\bar{C}B\bar{A} + \bar{D}C\bar{B}A$	20	CO3
------	---	----	-----

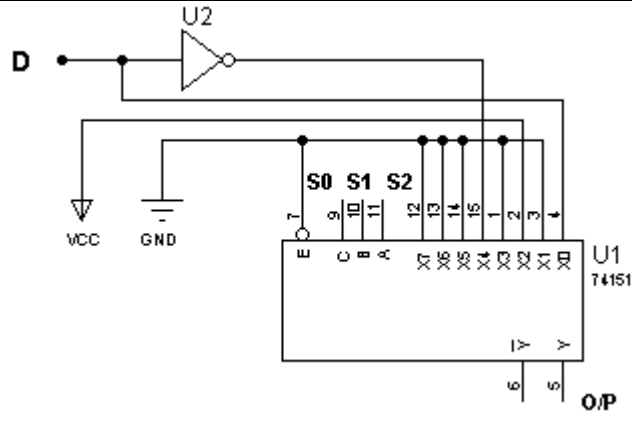

Name:

Enrolment No:



**UNIVERSITY OF PETROLEUM AND ENERGY STUDIES**  
**End Semester Examination, December 2018**  
SET-II

**Course:** Automation & Robotics Engineering (ECEG 2014)

**Semester:** I

**Programme:** M.Tech

**Time:** 03 hrs.

**Max. Marks:** 100

**Instructions:**

**SECTION A**

S. No.		Marks	CO
Q 1	Discuss the various filter circuits used for embedded circuits. Also draw the circuit.	4	CO5
Q 2	Discuss in brief the 5V buck converter power supply circuit used to drive robot.	4	CO2
Q 3	Discuss the role of capacitor and freewheeling diode in reducing back EMF from DC motor. Draw the circuit to support your answer.	4	CO2
Q 4	Discuss the rules to design the analog circuits in printed circuit boards.	4	CO3
Q 5	Discuss how the cost of processor increases if design is based on increasing speed of a processor. Calculation should base on mathematical expression.	4	CO3

**SECTION B**

Q 6	Design a BJT based amplifier using $\beta re$ model. Calculate the input and output impedances, voltage gain and current gain. Consider the $R_E$ (Emitter resistor) resistor if using self-bias or voltage divider bias based BJT amplifier.	10	CO1
Q 7	Below is the two PCB designs of power supply units. Comment on the flaws of the design		CO2

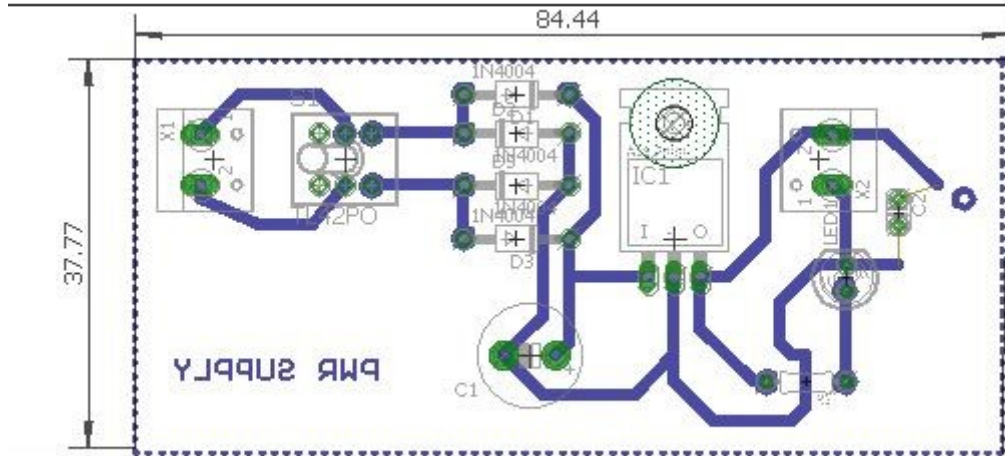


Fig 1

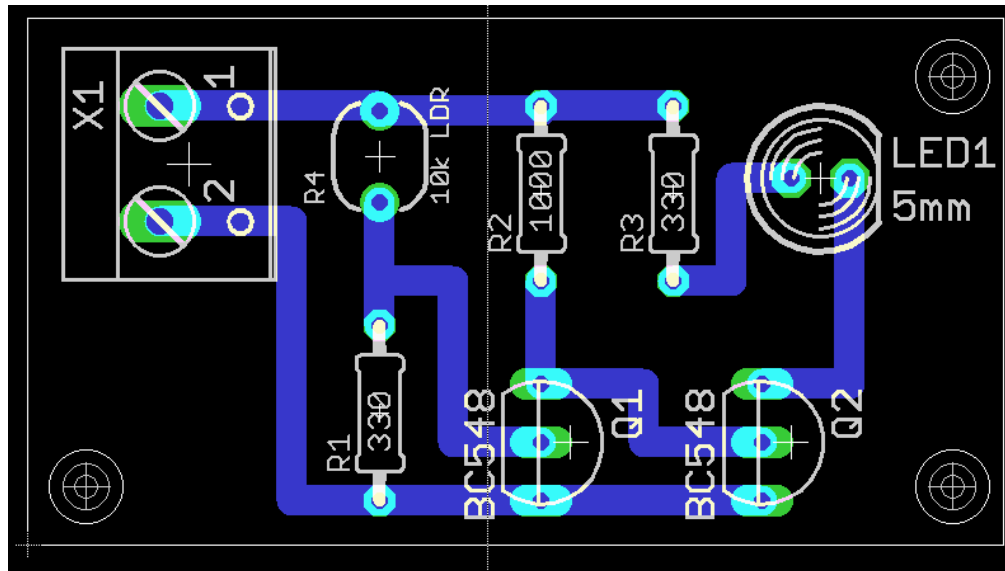


Fig 2

Q 8 Design and explain ULN2003 IC and explain the concept of using this driver IC to drive stepper motor.

10

CO3

Q 9 Apply the fundamental rules of designing printed circuit board and explain how the power supply section of PCB is designed and managed for 2A of current.

10

CO2

OR

Q 10 In a certain chemical processing plant, a liquid chemical is used in a manufacturing

10

CO3

process. The chemical is stored in three different tanks. A level sensor in each tank produces a high voltage when the level of chemical in the tank drops below a specified point.

Design a circuit that monitors the chemical level in each tank and indicates when the level in any two of the tanks drops below the specified point.

**SECTION-C**


Q 11 Design a white light (from flash light) tracking circuit for a Robot that will track the white light in real time.

**20 CO5**

Q 12 The circuit shows how an 8-bit MUX can be used to generate a four-variable logic function even though the MUX has only 3 SELECT inputs.

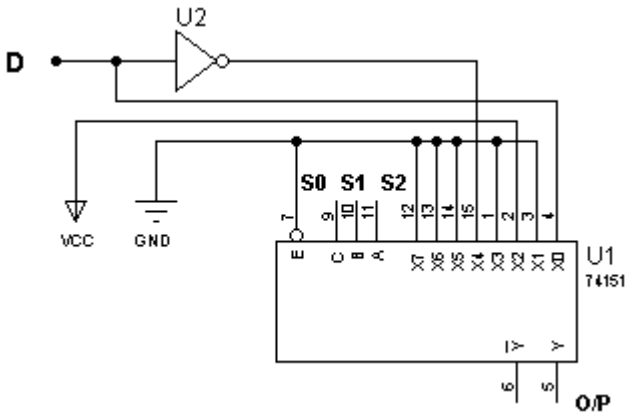- (c) Setup a truth table showing the output Y for the 16 possible combinations of input variables.
- (d) Write the sum-of-products expression for Y and simplify it to verify that

$$Y = \bar{C}B\bar{A} + D\bar{C}B\bar{A} + \bar{D}C\bar{B}A$$



**20 CO3**