

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, December 2018

Programme Name: B Tech ECE

Course Name : Network Analysis

Course Code : ECEG2020

Nos. of page(s) : 4

Semester : III

Time : 03 hrs

Max. Marks : 100

Instructions:

- Attempt all questions as per the requirement.
- Assume any data if required and indicate the same clearly. Unless otherwise indicated symbols and notations have their usual meanings.
- Strike off all unused blank pages

SECTION A (20 Marks)

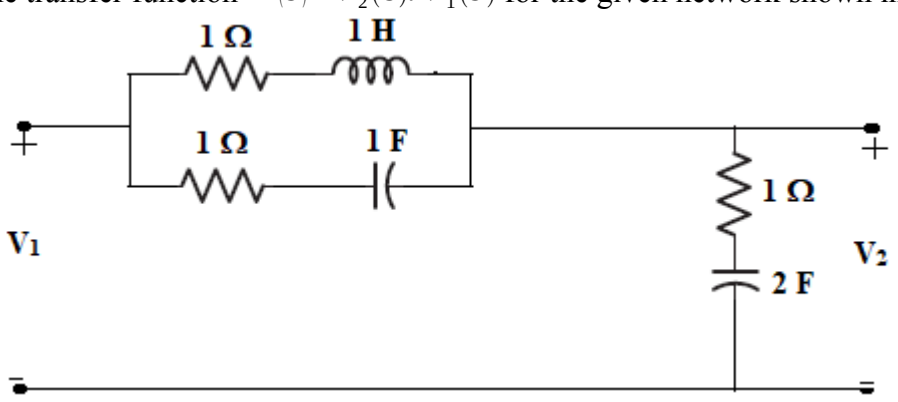
S.No.		Marks	CO																								
Q1	State the following network theorems: Thevenin's theorem and Tellegen's theorem.	4	CO1																								
Q2	Determine the number of possible trees of network represented with the following incidence matrix: <table border="1" data-bbox="203 1113 682 1270"><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>-1</td><td>0</td><td>1</td><td>-1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>-1</td><td>-1</td><td>0</td><td>1</td></tr><tr><td>-1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>-1</td></tr></table>	1	1	1	0	0	0	0	-1	0	1	-1	0	0	0	-1	-1	0	1	-1	0	0	0	1	-1	4	CO3
1	1	1	0	0	0																						
0	-1	0	1	-1	0																						
0	0	-1	-1	0	1																						
-1	0	0	0	1	-1																						
Q3	A 2-port network is represented by the following equations: $V_1 = 60 I_1 + 20 I_2$ $V_2 = 20 I_1 + 40 I_2$ Calculate the ABCD parameters for this network.	4	CO2																								
Q4	Write properties of Hurwitz polynomial.	4	CO4																								
Q5	Find the transfer function $H(s) = V_2(s)/V_1(s)$ for the given network shown in Fig.1 	4	CO5																								

Fig.1

SECTION B (40 Marks)

Q6 State superposition theorem and determine i_0 in the circuit shown in Fig.2 using superposition theorem.

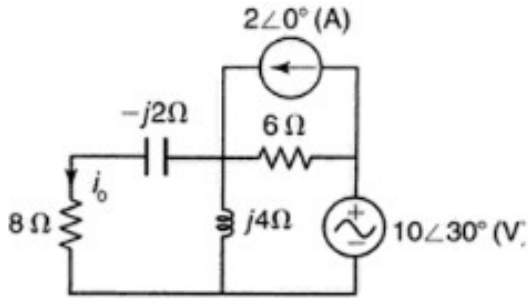


Fig.2

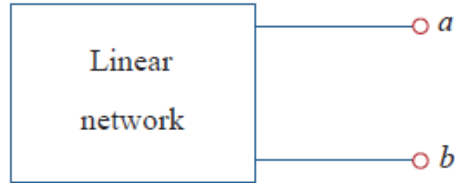


Fig.3

Or

The Thevenin's equivalent at terminals of the linear network shown in Fig.3 is to be determined by measurement. When a 10-kΩ resistor is connected to terminals a-b, the voltage is measured as 6 V. When a 30-kΩ resistor is connected to the terminals, is measured as 12 V. Determine:

- (a) the Thevenin's equivalent at terminals a-b,
- (b) when a 20-k_ resistor is connected to terminals a-b.

8

CO1

Q7 For the network shown in Fig.4 determine the z and y parameters

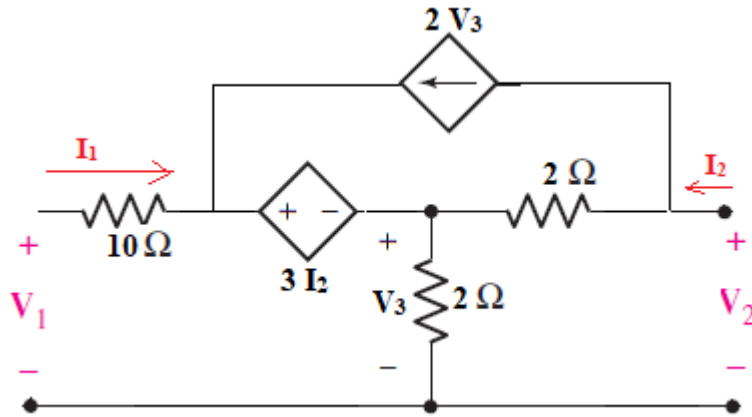


Fig.4

Or

The ABCD parameters of a two-port network shown in Fig.5 are $\begin{bmatrix} 4 & 20 \\ 0.1 & 2 \end{bmatrix}$. The output is connected to the variable load R_L for maximum power transfer. Calculate R_L and the maximum power transfer.

8

CO2

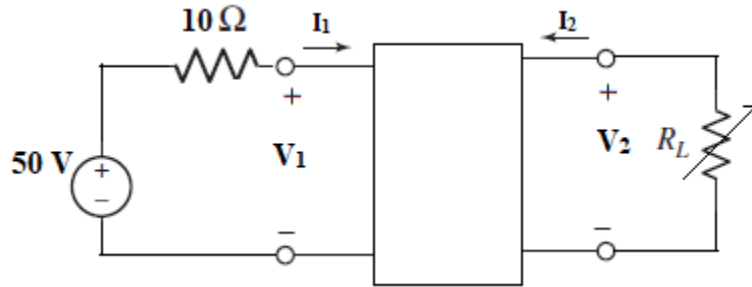


Fig.5

Q8 (a) Draw pole-zero plot for $V(s) = \frac{5s}{s^2 + 7s + 12}$. Determine the time domain expression $v(t)$ from its transform $V(s)$.

5+3

CO4

(b) Write the necessary conditions for network driving point impedance function.

Q9 Write incidence matrix and cut-set matrix of network shown in Fig.6

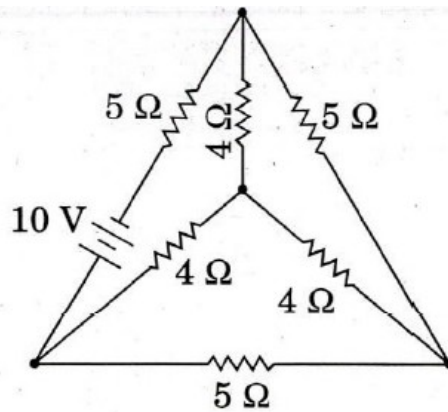


Fig.6

8

CO3

Q10 (a) What is positive real functions? Write necessary and sufficient conditions for testing positive real functions.

5+3

CO4

(b) Test whether the following polynomial are positive real or not.

$$F(s) = \frac{10(s+1)^2}{(s+2)(s^2-6s+5)}$$

Q11

(a) Find the resistance R_1 of Fig.7 such that the resistor R_4 will receive maximum power.

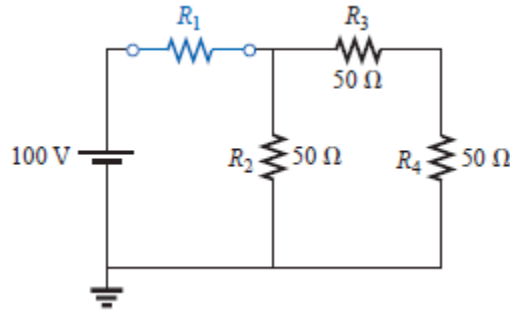


Fig.7

(b) For a two-port network shown in Fig.8 the z-parameters are $[Z] = \begin{bmatrix} 10 & -6 \\ -4 & 12 \end{bmatrix} \Omega$

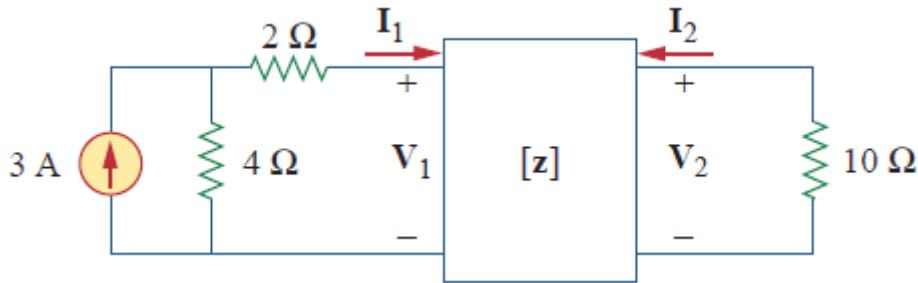


Fig.8

Calculate I_1 , I_2 , V_1 and V_2

10+10

CO2

Q12

Synthesize the following impedance function in Foster-I and Causer- II forms:

$$Z(s) = \frac{(s^2+4)(s^2+25)}{s(s^2+9)}$$

Or

A network function has poles at 0, -4, -6 and zeros at -2, -5. Taking the scaling factor to be 1, synthesize the function (i) as an impedance function in Foster's form and (ii) as an admittance function in Causer form.

20

CO4