



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, December 2017

Program: B.Tech(EE/BCT/IoT)
Subject (Course): Network theory
Course Code : ELEG 204
No. of page/s: 3

Semester – III
Max. Marks : 100
Duration : 3 Hrs


Attempt all questions.

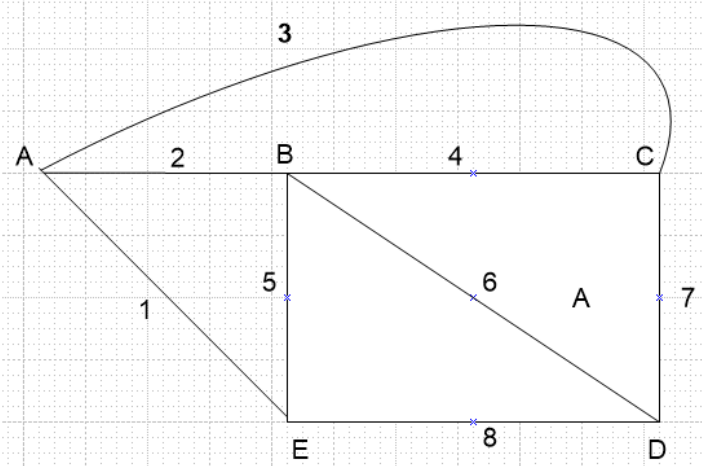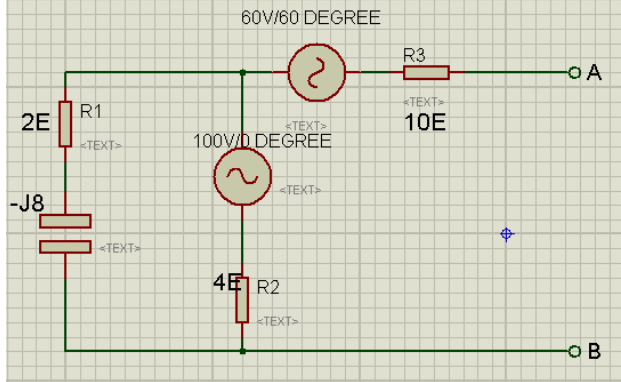SECTION A		Marks[20]	
1.	Determine the possible number of trees from figure[a] <div style="text-align: center; margin-top: 10px;">  <p style="text-align: center;">figure[a]</p> </div>	[5]	CO3
2.	Differentiate between tree and co-tree.	[5]	CO3
3.	Find the Thevenin's equivalent circuit at terminals AB of the circuit given in Figure[b] <div style="text-align: center; margin-top: 10px;">  <p style="text-align: center;">figure[b]</p> </div>	[5]	CO1
4.	Draw the equivalent circuit of a two-port network in terms of ABCD parameters. Also, derive the formula convert ABCD parameters in terms of h parameters.	[5]	CO1

SECTION B

Marks[40]

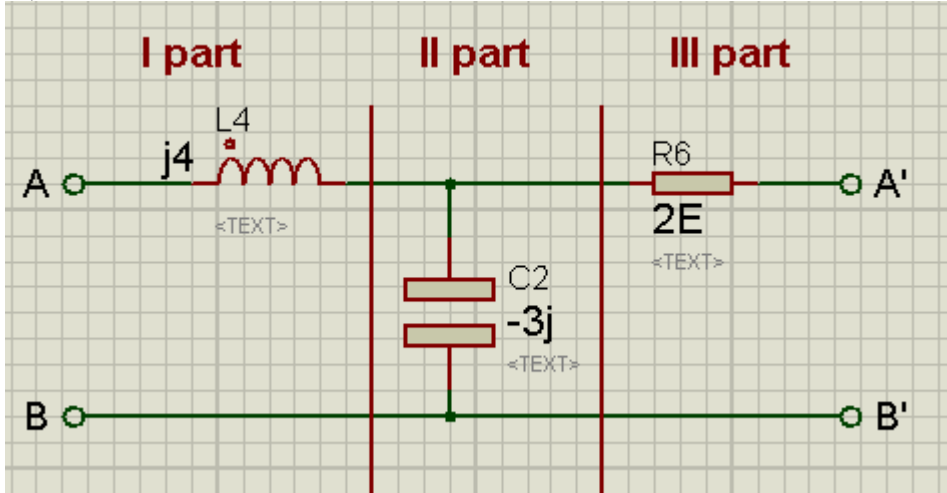5. Determine transmission parameters of a T network shown in figure [c] considering three parts I, II, III are connected in cascade.




Figure[c]

[10]

CO2

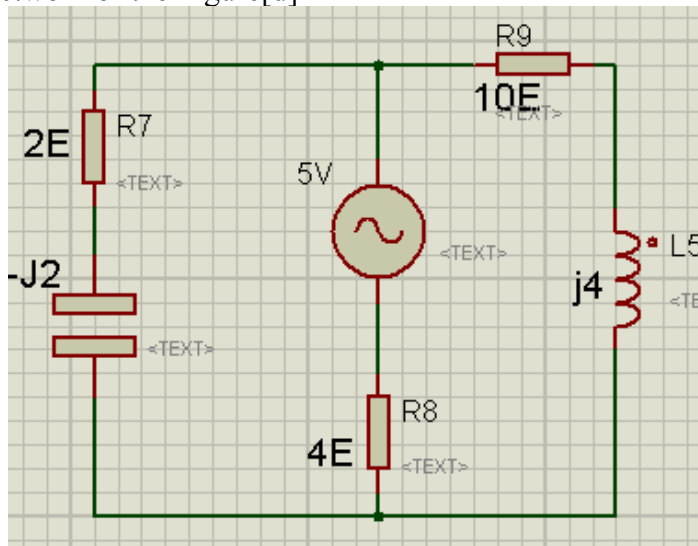6. Draw the Dual network of the Figure[d]



Figure[d]

[10]

CO4

7. Draw The Pole Zero diagram of given transfer function. Also find the time domain response of system using Pole-Zero diagram method and also verify it alternatively using residue method

$$H(s) = \frac{2s}{(s^2 + 4s + 8)}$$

[10]

CO3

8. Synthesize the given impedance function in Foster I and Foster II form

$$\frac{8(s^2 + 4)(s^2 + 25)}{s(s^2 + 16)}$$

[5+5]

CO4


SECTION C

Marks[40]

9. Design the f-loop matrix and f-loop equations, for the network shown in figure [e].

[20]

CO3

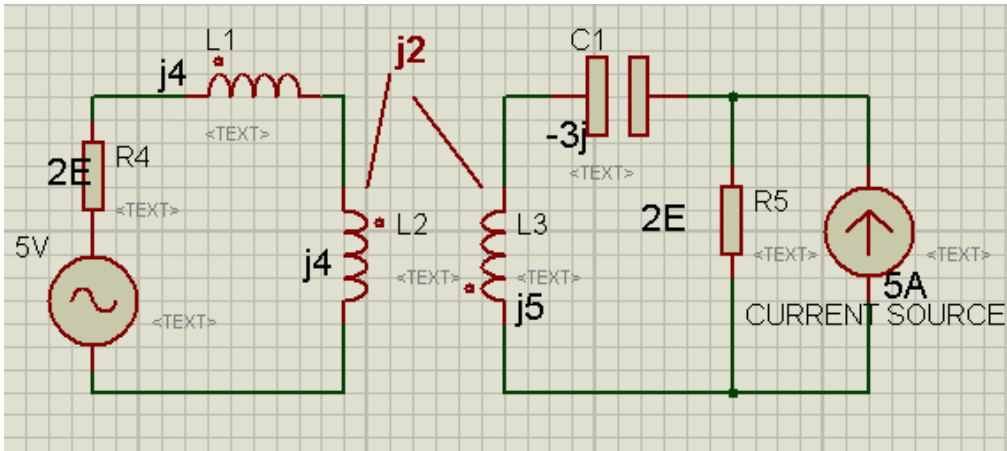

Figure[e]

10. Synthesize the given function $F(s) = \frac{3(s+2)(s+4)}{s(s+3)}$ in a **foster Form I&II** and a **Cauer Form I&II**, if

[20]

CO4

- (a) F(s) is an impedance function
- (b) F(s) is an admittance function

Roll No: -----


UNIVERSITY OF PETROLEUM AND ENERGY STUDIES


End Semester Examination, December 2017

Program: B.Tech(EE/BCT/IoT)
Subject (Course): Network theory
Course Code : ELEG 204
No. of page/s: 3

Semester – III
Max. Marks : 100
Duration : 3 Hrs

Attempt all questions.

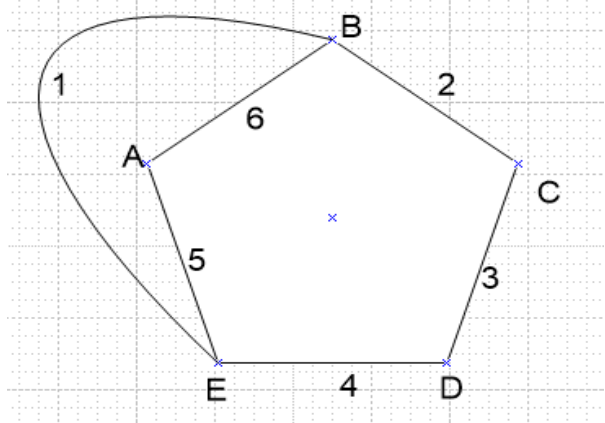SECTION A		Marks[20]	
1.	Determine the possible number of trees from figure[a] <div style="text-align: center; margin: 10px 0;">  <p>figure[a]</p> </div>	[5]	CO3
2.	Differentiate between twigs and links.	[5]	CO3
3.	Find the Norton equivalent circuit at terminals AB of the circuit given in Figure[b]	[5]	CO1

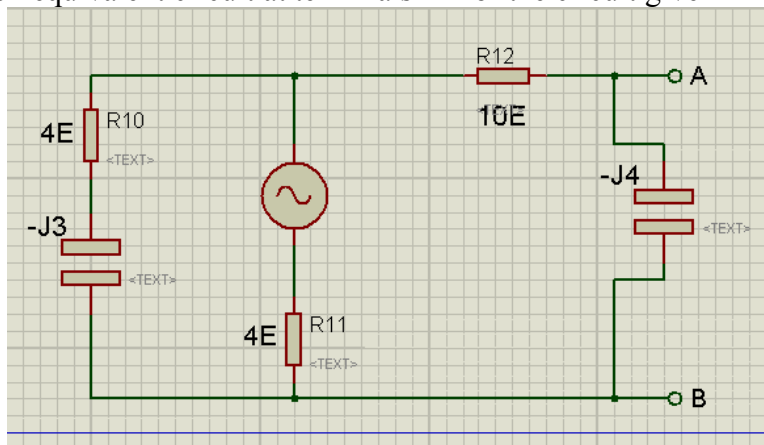


figure[b]

4. Draw the equivalent circuit of a two-port network in terms of Z parameters. Also, derive the formula convert Z parameters in terms of Y parameters. [5] CO1

SECTION B

Marks[40]

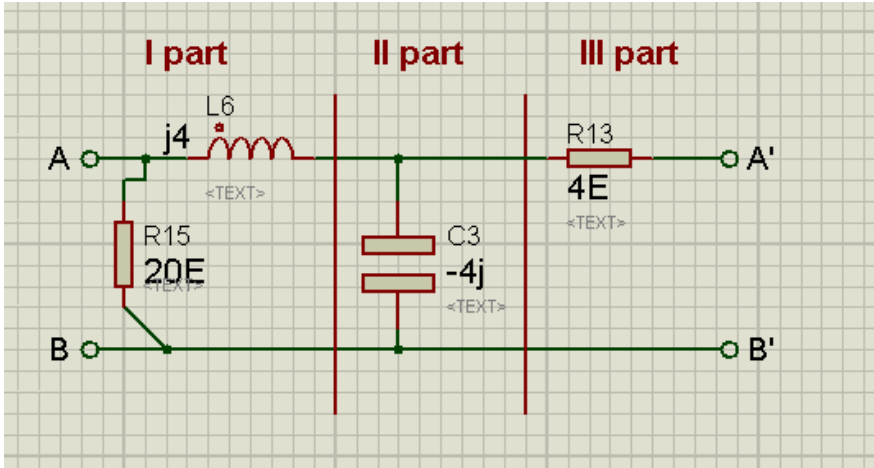5. Determine transmission parameters of a T network shown in figure [c] considering three parts I, II, III are connected in cascade.




Figure[c]

[10]

CO2

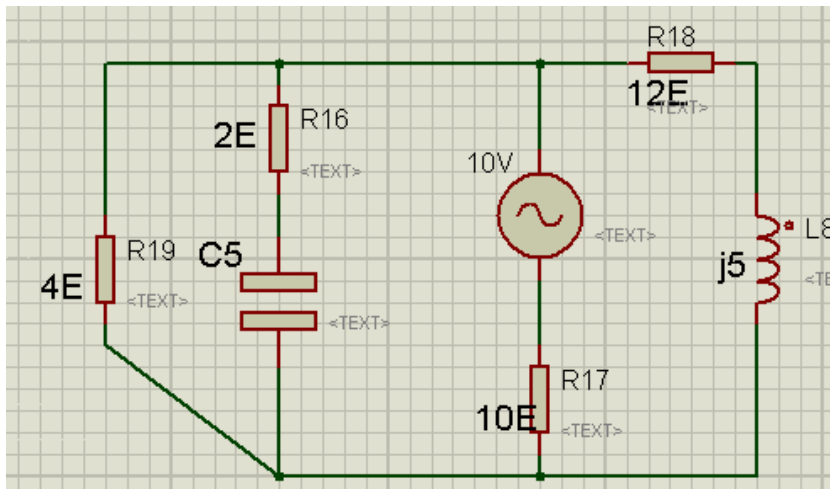6. Draw the Dual network of the Figure[d]. also discuss the properties to form the dual graph.



Figure[d]

[10]

CO4

7. Draw The Pole Zero diagram of given transfer function. Also find the time domain response of system using Pole-Zero diagram method and also verify it alternatively using residue method

$$H(s) = \frac{s^2 + 4s + 3}{(s^2 + 2s)}$$

[10]

CO3

8. Synthesize the given impedance function in Foster I and Cauer I form

[5+5]

CO4

$$\frac{2(s^2+1)(s^2+9)}{s(s^2+4)}$$


SECTION C

Marks[40]

9. Design the f-loop matrix and f-loop equations, for the network shown in figure [e]

[20]

CO3

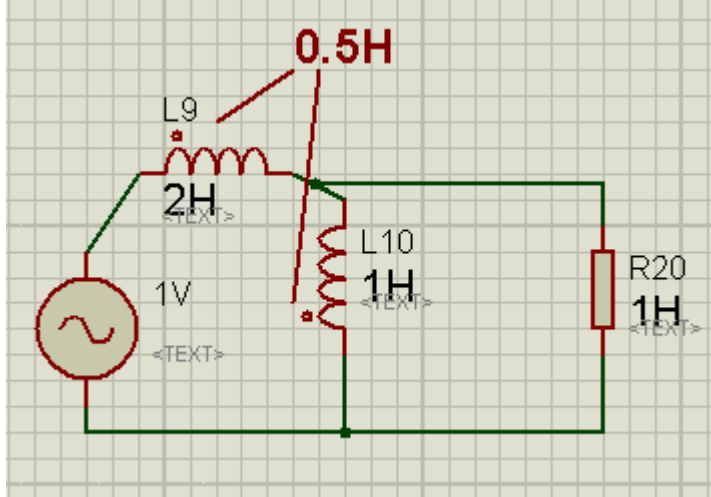

Figure[e]

10. Explore the R-L representation of (a) Foster I and II (b) Cauer I and II for an impedance function, given by $F(s) = \frac{s(s+2)(s+5)}{(s+1)(s+4)}$

[20]

CO4