

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES



End Semester Examination, December 2017

Program: B Tech.(Mechatronics Engineering)
Subject (Course): Analog and Digital Electronics
Course Code :GNEG291
No. of page/s:

Semester –III
Max. Marks : 100
Duration: 3 Hrs

NOTE: Attempt all questions

Part A

[5×4 = 20]


1. Simplify the Boolean Expression $F(W,X,Y,Z) = \sum(1,3,7,11,15) + \sum d(0,2,5)$ with the help of K-Map.
2. Realize EX-NOR gate from NAND Gate and draw its truth table by verifying the Boolean expression.
3. Convert from one number system to another.
 - a. $(37.4)_{16} = (?)_{10}$
 - b. $(ECE)_{16} = (?)_{10}$
 - c. $(754.23)_8 = (?)_2$
 - d. $(FACE)_{16} = (?)_8$
4. In a 4-bit ripple counter propagation delay of ripple counter is 25 ns then maximum clock frequency that can be applied to the counter is.....?

Part B

[10×4 = 40]

5. Implement 4-bit Look Ahead Carry Adder with the help of AND-OR-EXOR gates and if all logic gates have propagation delay, then calculate the delay at Carry and Sum.
6. Implement $f(A,B,C) = \sum m(0,1,5,6,7)$ using 4x1 MULTIPLEXER with A and C as control variable.
7. Develop Full Adder using 3x8 Decoder and draw its logic diagram.

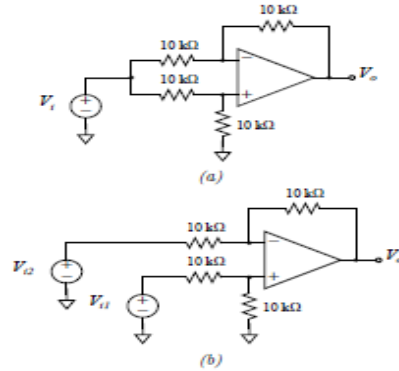8. Determine V_{out} for the two connections shown in below Figure. Assume $V_1 = 3V$, $V_a = 2V$ and $V_b = 3V$.



Part C

[2×20 = 40]

9. A clocked X-Y flip flop is defined with two inputs, X and Y is in addition to the clock input. The flip flop functions as follows:
- If XY=00, the flip flop changes state with each clock pulse.
 - If XY=01, the flip flop state Q becomes '1' with the next clock pulse.
 - If XY=10, the flip flop state Q becomes '0' with the next clock pulse.
 - If XY=11, the change of state occurs with the clock pulse.
- a. Write a truth table for the XY flip flop.
 - b. Write the Excitation tables for the XY flip flop.
 - c. It is desirable to convert a J-K flip flop into X-Y flip flop by adding some external gates, if necessary. Design a circuit to show how you will implement X-Y flip flop using J-K flip flop.
10. Design a circuit using op-amp to produce a square wave output whose output does not have any stable state and the Output has two Quasi-Stable states where output keeps on changing its own from 1state to another state and Vice Versa.

Roll No: -----

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES



End Semester Examination, December 2017

Program: B Tech.(Mechatronics Engineering)
Subject (Course): Analog and Digital Electronics
Course Code :GNEG291
No. of page/s:

Semester –III
Max. Marks : 100
Duration: 3 Hrs

NOTE: Attempt all questions

Part A

[5×4 = 20]


- Convert from one number system to another.
 - $(37.4)_{16} = (?)_{10}$
 - $(FACE)_{16} = (?)_{10}$
 - $(754.23)_8 = (?)_2$
 - $(CAD)_{16} = (?)_8$
- Simplify the Boolean Expression $F(W,X,Y,Z) = \sum(1,3,7,11,15) + \sum d(0,2,5)$ using K-Map.
- Realize EX-NOR gate from NAND Gate and draw its truth table by verifying the Boolean expression.
- In a 4-bit ripple counter propagation delay of ripple counter is 25 ns then maximum clock frequency that can be applied to the counter is.....?

Part B

[10×4 = 40]

- Implement 4-bit Look Ahead Carry Adder with the help of AND-OR-EXOR gates and if all logic gates have propagation delay, then calculate the delay at Carry and Sum.
- Implement $f(A,B,C) = \sum m(0,1,5,6,7)$ using 4x1 MULTIPLEXER with A and C as control variable.

 7. Determine V_{out} for the two connections shown in below Figure. Assume $V_1 = 3V$, $V_a = 2V$ and $V_b = 3V$.



8. Develop Full Adder using 3x8 Decoder and draw its logic diagram.

Part C

[2×20 = 40]

9. Design a circuit using op-amp to produce a square wave output whose output does not have any stable state and the Output has two Quasi-Stable states where output keeps on changing its own from 1state to another state and Vice Versa.
10. A new clocked X-Y flip flop is defined with two inputs, X and Y is in addition to the clock input. The flip flop functions as follows:
 If $XY=00$, the flip flop changes state with each clock pulse.
 If $XY=01$, the flip flop state Q becomes '1' with the next clock pulse.
 If $XY=10$, the flip flop state Q becomes '0' with the next clock pulse.
 If $XY=11$, the change of state occurs with the clock pulse.
- Write a truth table for the XY flip flop.
 - Write the Excitation table for the XY flip flop.
 - It is desirable to convert a J-K flip flop into X-Y flip flop by adding some external gates, if necessary. Design a circuit to show how you will implement in X-Y flip flop using J-K flip flop.
