

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, December 2017

Program: B. Tech(EE)
Subject (Course): LIC
Course Code : ELEG263
No. of page/s: 01

Semester – V
Max. Marks : 100
Duration : 3 Hrs

Attempt all questions.

SECTION A		Marks[20]	
1.	Describe the virtual ground concept for OP AMP IC uA741.	[5]	CO3
2.	Elaborate the working of peak detector with the help of circuit and waveform	[5]	CO3
3.	Discuss the effect of negative feedback on input and output resistance of OP AMP.	[5]	CO2
4.	Describe the output voltage of an differentiator circuit with OP AMP and discuss the frequency response of ideal & practical differentiator circuit.	[5]	CO2
SECTION B		Marks[40]	
5.	Draw a dual input, balanced output differential amplifier with $R_C=2.2\text{ K}\Omega$, $R_E=4.7\text{ K}\Omega$, $R_{in1}=R_{in2}=50\ \Omega$, $+V_{CC}=10\text{V}$, $-V_{EE}=-10\text{V}$ and $\beta_{dc}=\beta_{ac}=100$ and $V_{BE}=0.715\text{V}$ (a) Determine the I_{CQ} and V_{CEQ} values (b) Determine the voltage gain (c) Determine the input and output resistance	[10]	CO1
6.	An 8bit A/D converter accepts an input signal of range 0 to 10V. (a) Calculate the minimum value of the input voltage required to generate a change of 1 LSB. (b) What input voltage will generate all 1s at the A/D converter output? (c) Calculate the digital output for an input voltage of 4.8V.	[10]	CO4
7.	(a) Elaborate circuit of Anti- logarithmic amplifier. (b) Discuss Sample and hold circuit with OP AMP.	[5+5]	CO3
8.	(a) Justify the non-inverting configuration of OP AMP is voltage series feedback. (b) Derive the expression for voltage to current converter.	[5+5]	CO4
SECTION C		Marks[40]	
9.	Design a wide band pass filter with $f_L=200\text{ Hz}$, $f_H=1\text{KHz}$ and passband gain of 4. Also calculate the quality factor of designed filter and draw the frequency response of the filter.	[20]	CO3
10.	(a) Design and draw an astable multivibrator using IC555 timer for a frequency of 1KHz and a duty cycle of 70%. (b) Design and discuss the working of a power supply with 5V DC output with the help of voltage regulator and precision full wave rectifier.	[10+10]	CO4

Roll No: -----

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, December 2017

Program: B. Tech(EE)
Subject (Course): LIC
Course Code : ELEG263
No. of page/s: 01

Semester – V
Max. Marks : 100
Duration : 3 Hrs

Attempt all questions.

SECTION A		Marks[20]	
1.	Draw and discuss the working of successive approximation analog to digital converter.	[5]	CO4
2.	Discuss and draw precision full wave rectifier with OP-AMP	[5]	CO3
3.	For 741C non inverting OP-AMP with $R_i=1\text{ K}\Omega$, $R_F=10\text{ K}\Omega$, $A=200000$, $R_i=2\text{ M}\Omega$, $R_o=75\text{ }\Omega$, $f_o=5\text{ Hz}$, supply voltages= $\pm 15\text{ V}$, output voltage swing= $\pm 13\text{ V}$. Compute the A_F , R_{iF} , R_{oF} , f_F , V_{oot}	[5]	CO2
4.	Justify the inverting configuration of OP AMP is voltage shunt feedback.	[5]	CO2
SECTION B		Marks[40]	
5.	For a single input, balanced output differential amplifier with $R_C=2.2\text{ K}\Omega$, $R_E=4.7\text{ K}\Omega$, $R_{in1}=R_{in2}=50\text{ }\Omega$, $+V_{cc}=10\text{ V}$, $-V_{EE}=-10\text{ V}$ and $\beta_{dc}=\beta_{ac}=100$ and $V_{BE}=0.715\text{ V}$ (a) Calculate the I_{CQ} and V_{CEQ} values (b) Discuss the voltage gain (c) Determine the input and output resistance	[10]	CO1
6.	Elaborate digital to analog converter and draw & explain the working of – (a) Binary weighted resistors (b) R and 2R resistors	[10]	CO4
7.	Design a circuit with output as summing circuit, scaling circuit and average circuit should be 12V, 6V and 4V respectively.	[10]	CO3
8.	(a) Derive the expression for current to voltage converter. (b) Elaborate circuit of logarithmic amplifier	[5+5]	CO4
SECTION C		Marks[40]	
9.	Design a second order high pass filter with $f_L=1\text{ KHz}$ and passband gain of 1.58. Draw the frequency response of the designed filter.	[20]	CO3
10.	i.) Design and discuss working of a sawtooth waveform generator for 10V peak and frequency of 200Hz. Assume $V_i=2\text{ V}$ and $V_{ref}=10\text{ V}$. ii.) Design a monostable multivibrator with IC555 timer for a pulse period of 1ms.	[10+10]	CO4