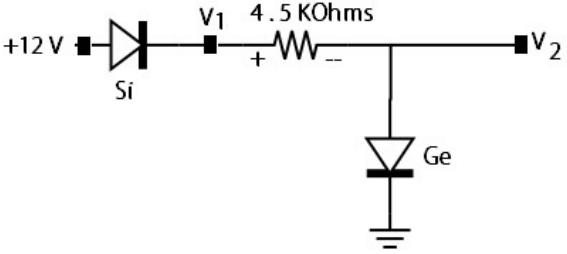


Name:	
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, Dec 2020

Programme Name: B.TECH ECE Course Name: Analog Electronics I Course Code: ECEG 2011 Nos. of page(s): 2 Instructions: All questions are compulsory	Semester: III Time: 03 hrs Max. Marks: 100
---	---


SECTION A

S. No.		Marks	CO
Q 1	Fill in the Blanks 1.a The input Impedance of amplifier should be veryas possible. 1.b Emitter follower configuration has.....voltage gain. 1.c CE configuration output is differ by Phase shift. 1.d For switching action of BJT the biasing region of the BJT should be in..... region	5	CO1
Q 2	For the circuit shown in fig 1, determine V_1 and V_2 <div style="text-align: center;">  </div> <p style="text-align: center;">Fig. 1</p>	5	CO1
Q 3	Define the thermal runaway condition in BJTs and why FET are more preferable over BJTs.	5	CO2
Q 4	Why the DC operating point is preferred to get biased at middle of DC load line.	5	CO1
Q5	Choose the correct answer (MCQ type): 5.1 The action of JFET in its equivalent circuit can best be represented as a A. Current controlled Current source B. Current controlled voltage source C. Voltage controlled voltage source D. voltage controlled current source 5.2 The current gain of a bipolar transistor drops at high frequencies because of	5	CO2

	<p>A. Transistor capacitances B. High current effects in the base C. Parasitic inductive elements D. The early effect</p> <p>5.3 Most of the linear ICs are based on the two-transistor differential amplifier because of its</p> <p>A. Input voltage dependent linear transfer characteristic B. High voltage gain C. High input resistance D. High CMRR</p>		
--	--	--	--

Q6	How temperature affects the performance of the Amplifier and what is the role of different biasing configuration used for amplification network.	5	CO3
----	--	---	-----

SECTION B

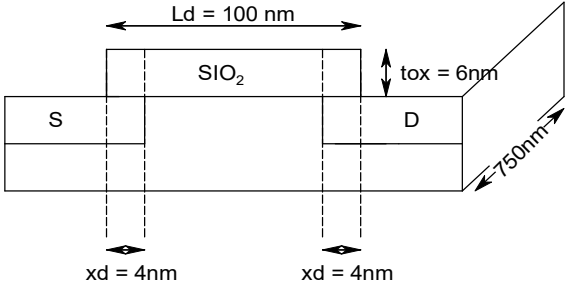Q7	<p>Compute the Gate capacitance C_G, gate to drain capacitance C_{GD}, gate to source capacitance for the Fig. 1. Consider the overlapping capacitances $C_{GSO} = C_{GDO} = 5 \text{ fF/m}^2$. What will be effects on these capacitances when horizontal dimension are scaled by 1/4 and vertical dimensions by 1/3.</p> <div style="text-align: center;">  <p>The diagram shows a cross-section of a MOSFET. The gate length is labeled as $L_d = 100 \text{ nm}$. The gate oxide thickness is $t_{ox} = 6 \text{ nm}$. The channel length is 750 nm. The source and drain regions have a width of $x_d = 4 \text{ nm}$. The gate is labeled SiO_2. The source and drain regions are labeled S and D respectively.</p> </div> <p style="text-align: center;">Fig. 1</p>	10	CO2
----	---	----	-----

Q 8	<p>The fixed-bias configuration shown in Fig. 2 having an operating point defined by $V_{GSQ} = 2 \text{ V}$ and $I_{DQ} = 5.625 \text{ mA}$, with $I_{DSS} = 10 \text{ mA}$ and $V_{GSOFF} = -8 \text{ V}$. The network is redrawn as Fig with an applied signal V_i. The value of y_o is provided as 50 uS.</p> <p>(a) Determine g_m. (b) Find r_d. (c) Determine Z_i. (d) Calculate Z_o. (e) Determine the voltage gain A_v.</p>	10	CO3
-----	---	----	-----

 


Fig. 2

- Q9 A self bias configuration is shown in Fig. 3 has an operating point defined by $V_{GS} = -2.6$ V and $I_{DQ} = 2.6$ mA. Determine the followings for y_{os} is given as $20 \mu\text{S}$
- Tranconductance
 - Rd
 - Zi
 - Compute A_v with and without effects of r_d . compare the results

 


Fig. 3

10

CO3

- Q10 (a) Determine the operating point of the given amplifier as shown in Fig 4 under DC analysis? Evaluate the following performance parameters of the given CE amplifier below
- Find Z_i and Z_o .
 - Calculate A_v and A_i .

10

CO2

 


Fig. 4


Q11 Differentiate between Enhancement type and Depletion type MOSFET? Why it is considered high input impedance for the amplification action and how MOSFETs are suitable for this action.

10

CO4

SECTION-C

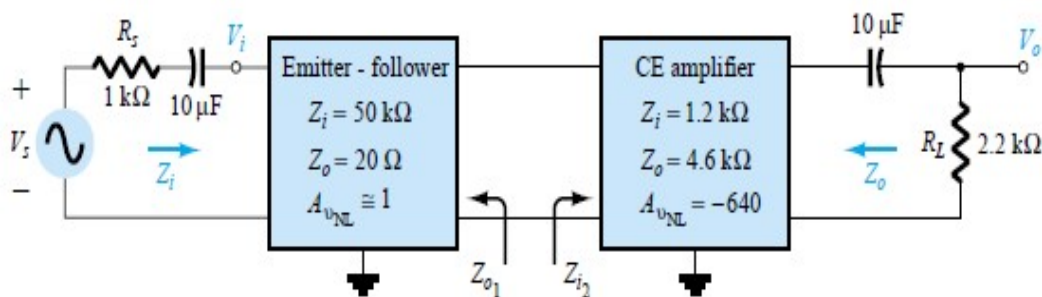Q 12 Consider the cascade amplifier configuration for Common emitter of figure given below, determine the following? :
 (a) The loaded voltage gain of each stage.
 (b) The total gain of the system, A_v .
 (c) The total gain of the system, A_i .



20

CO4