

Name:	
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2021

Course: Network Analysis	Semester: III
Program: B. Tech- ECE	Time: 03 hrs.
Course Code: ECEG -2020	Max. Marks: 100

Instructions: (i) Attempt all the sections.


SECTION-A (20 Marks)


Each Question will carry 4 Marks
Instruction: Write briefly (5-6 lines)

S. No	Question	CO
Q 1	What are the open circuit impedance parameters of a two-port network? Why are they so called?	CO2
Q 2	Briefly define for: (i) Rank of Graph (ii) Planner Graph (iii) Tree (iv) Twig	CO3
Q 3	Explain minimum two properties of Hurwitz polynomial.	CO4
Q 4	Define Y-parameters. Determine the relationship between the Z and Y parameters.	CO2
Q 5	Define (i) Transfer impedance function (ii) Current transfer function	CO3

SECTION-B (40 Marks)


Each question will carry 10 marks
Instruction: Attempt all the questions

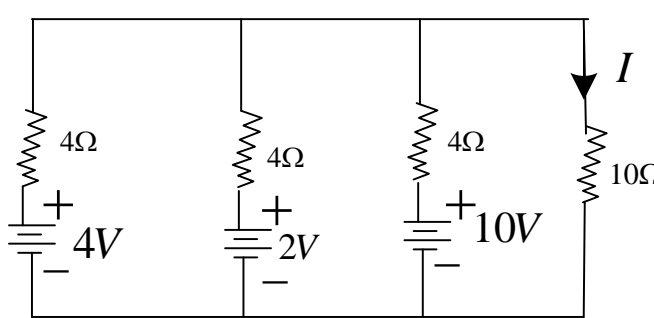Q 1	Determine the load current using Millman's theorem. Network shown in Figure. <div style="text-align: center; margin: 10px 0;">  </div>	CO1
Q 2	Find the Thevenin's equivalent circuit for the electrical circuit given in the bridge network as,	CO1

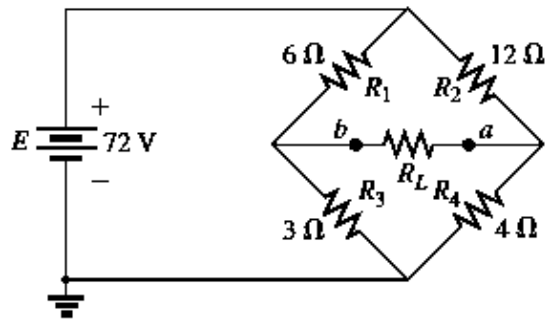


Q 3 Find the open circuit driving point impedance at terminals 1-1' of the ladder work shown in Fig.

CO3

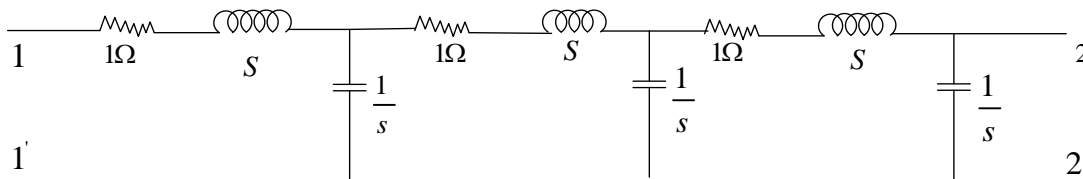


OR

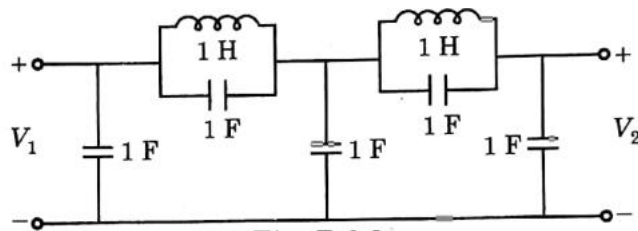For the given network circuit, calculate the voltage ratio transfer function



Q 4 **Attempt both the parts:**
 (a) With reference to Figure, draw the graph and write down the tie-set matrix. Obtain the network equilibrium equations in matrix using Kirchoff's Voltage Law (KVL).

CO4
(5+5)

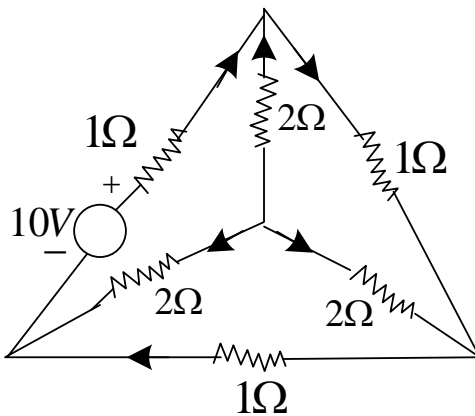

(b) Incidence matrix of a graph is given below. Draw the directed graph:

Nodes	Branches \longrightarrow						
	1	2	3	4	5	6	7
(1)	-1	0	-1	1	0	0	1
(2)	0	-1	0	-1	0	-1	0
(3)	1	1	0	0	-1	1	0
(4)	0	0	1	0	1	0	-1

SECTION-C (40 Marks)


Each Question carries 20 Marks.

Instruction: Write long answer.

Q 1

Attempt both the parts:

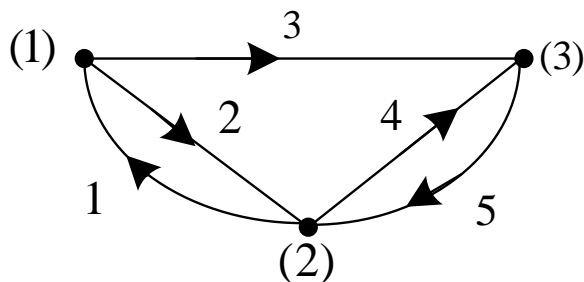(a) Design all the possible trees. Also, determine the incidence matrix for the given graph.



(b) Show the function $F(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)}$ is positive real function or not?


(c) Check whether the given polynomial $P(s) = s^4 + s^3 + 2s^2 + 4s + 1$ is Hurwitz or not?

CO4

(10+5+5)

Q-2

Find the expression of voltage transfer function $G_{21}(s) = \frac{V_2(s)}{V_1(s)}$ for the network shown in Figure

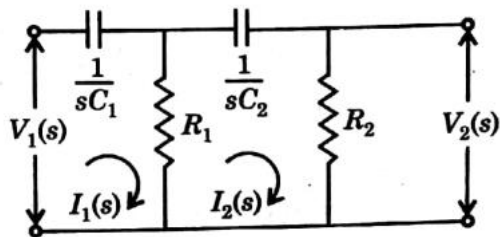

CO3

(20)
