


Name:			
Enrolment No:			
<b>UNIVERSITY OF PETROLEUM AND ENERGY STUDIES</b> <b>End Semester Examination, December 2022</b>			
<b>Course: Electrical machines</b> <b>Program: B Tech Mechatronics</b> <b>Course Code: EPEG 2013</b>		<b>Semester: III</b> <b>Time : 03 hrs.</b> <b>Max. Marks: 100</b>	
<b>SECTION A</b> <b>(5Qx4M=20Marks)</b>			
S. No.		Marks	CO
Q 1	What are the essential parts of a transformer?	4	CO1
Q 2	Which test on a 1-phase transformer gives the iron losses, also justify your answer.	4	CO1
Q 3	Sketch the characteristics of a DC shunt motor and give the practical applications.	4	CO2
Q 4	Why core of a transformer is laminated and insulated?	4	CO1
Q 5	State the types of dc motors. What is the basis of the classification?	4	CO2
<b>SECTION B</b> <b>(4Qx10M= 40 Marks)</b>			
Q.6	A 220 V, 50 Hz, 6-pole, single-phase induction motor has the following circuit model parameters: $R_{1m} = 3.6 \text{ ohm}$ ( $X_{1m} + X_2$ ) = 15.6 ohm $R_2 = 6.8 \text{ ohm}$ $X = 96 \text{ ohm}$ The rotational losses of the motor are estimated to be 75 W. At a motor speed of 940 rpm, determine the line current, power factor, shaft power and efficiency.	10	CO4
Q.7	Develop the phasor diagram of a single-phase transformer under load condition. Assume lagging power factor load.	10	CO4
Q.8	With the help of neat sketch explain the construction, working principle of a DC machine.	10	CO3
Q.9	Derive the expression for air gap power, torque and power output for an induction machine.	10	CO5
<b>SECTION-C</b> <b>(2Qx20M=40 Marks)</b>			
Q. 10	The following test results were obtained for a 20 kVA, 50 Hz, 2400/240 V distribution transformer:	20	CO4

	<p>Open-circuit test (LV): 240 V, 1.066 A, 126.6 W  Short-circuit test (HV): 57.5 V, 8.34 A, 284 W</p> <p>(a) When the transformer is operated as a stepdown transformer with the output voltage equal to 240 V, supplying a load at unity power factor, determine the maximum efficiency and the unity power factor load at which it occurs.</p> <p>(b) Determine the power-factor of the rated load, supplied at 240 V, such that the terminal voltage observed on reducing the load to zero is still 240 V.</p>		
Q. 11	<p>A 4-pole series-wound fan motor draws an armature current of 50 A, when running at 2000 rpm on a 230 V dc supply with four field coil connected in series. The four field coils are now connected in two parallel groups of two coils in series. Assuming the flux/pole to be proportional to the exciting current and load torque proportional to the square of speed, find the new speed and armature current. Neglect losses. Given: armature resistance = 0.2 ohm, resistance of each field coil = 0.05 ohm.</p> <p style="text-align: center;"><b>OR</b></p> <p>A 230 V dc shunt motor having armature resistance of 2 ohm draws an armature current of 5 A to drive a constant torque load at 1250 rpm. At no load it draws a current of 1 A.</p> <p>(a) A resistance of 15 ohm is added in series to the armature. Find the motor speed with load torque as above.</p> <p>(b) A resistance of 15 ohm is shunted across the armature and 10 ohm in series with the supply line. Calculate the load speed.</p>	<b>20</b>	<b>CO5</b>