
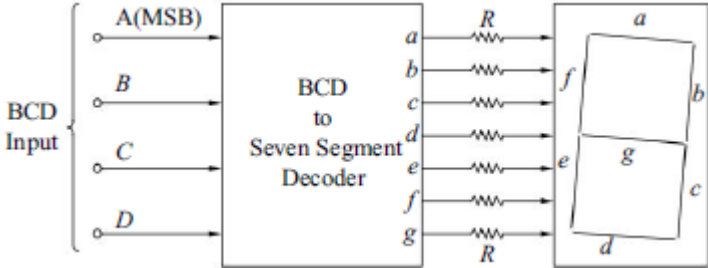
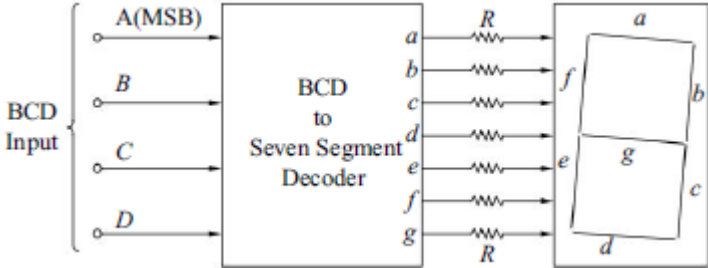
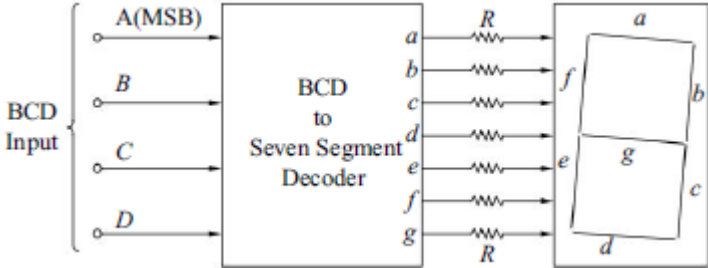


<b>Name:</b>																																			
<b>Enrolment No:</b>																																			
<div>UPES</div> <div>End Semester Examination, May 2025</div> <div><div>Course: Digital Electronics</div><div>Semester: 2</div><div>Program: B.Tech_CS_CSE</div><div>Time: 03 hrs.</div><div>Course Code: ECEG1012</div><div>Max. Marks: 100</div></div> <div>Instructions:</div> <div><ul style="list-style-type: none"><li>Electronic gadgets are not allowed during the examination except a scientific calculator.</li><li>Carrying any material related to the subject of examination and bags are prohibited during the examination.</li><li>Exchange of material is prohibited.</li></ul></div>																																			
<div>SECTION A</div> <div>(5Qx4M=20Marks)</div> <table><tr><th>S. No.</th><th></th><th>Marks</th><th>CO</th></tr><tr><td>Q 1</td><td>a. Express XNOR operation using 2-input NOR gates b. Express OR operation using CMOS logic</td><td>2+2</td><td>CO1</td></tr><tr><td>Q2</td><td>Differentiate multiplexers and encoders with labeled diagrams.</td><td>4</td><td>CO1</td></tr><tr><td>Q3</td><td>Distinguish between synchronous sequential circuits and asynchronous sequential circuits.</td><td>4</td><td>CO2</td></tr><tr><td>Q4</td><td>Draw the truth table for BCD to Excess-3 converter and express the outputs (Excess-3) in terms of min-terms and don't cares.</td><td>4</td><td>CO3</td></tr><tr><td>Q5</td><td>Define opcode and operand with an example.</td><td>4</td><td>CO4</td></tr><tr><td></td><td></td><td></td><td></td></tr></table> <div>SECTION B</div> <div>(4Qx10M= 40 Marks)</div> <table><tr><td>Q6</td><td><div>Consider the following diagram of BCD-to-7-Segment decoder.</div><div></div><div>a. Write the truth table for the BCD-to-7 Segment Decoder b. Derive an expression for the segment 'g' of the 7-segment display.</div></td><td>10</td><td>CO2</td></tr></table>				S. No.		Marks	CO	Q 1	a. Express XNOR operation using 2-input NOR gates b. Express OR operation using CMOS logic	2+2	CO1	Q2	Differentiate multiplexers and encoders with labeled diagrams.	4	CO1	Q3	Distinguish between synchronous sequential circuits and asynchronous sequential circuits.	4	CO2	Q4	Draw the truth table for BCD to Excess-3 converter and express the outputs (Excess-3) in terms of min-terms and don't cares.	4	CO3	Q5	Define opcode and operand with an example.	4	CO4					Q6	<div>Consider the following diagram of BCD-to-7-Segment decoder.</div> <div></div> <div>a. Write the truth table for the BCD-to-7 Segment Decoder b. Derive an expression for the segment 'g' of the 7-segment display.</div>	10	CO2
S. No.		Marks	CO																																
Q 1	a. Express XNOR operation using 2-input NOR gates b. Express OR operation using CMOS logic	2+2	CO1																																
Q2	Differentiate multiplexers and encoders with labeled diagrams.	4	CO1																																
Q3	Distinguish between synchronous sequential circuits and asynchronous sequential circuits.	4	CO2																																
Q4	Draw the truth table for BCD to Excess-3 converter and express the outputs (Excess-3) in terms of min-terms and don't cares.	4	CO3																																
Q5	Define opcode and operand with an example.	4	CO4																																
Q6	<div>Consider the following diagram of BCD-to-7-Segment decoder.</div> <div></div> <div>a. Write the truth table for the BCD-to-7 Segment Decoder b. Derive an expression for the segment 'g' of the 7-segment display.</div>	10	CO2																																

Q7	Simplify the following Boolean expression using the Quine-McCluskey (QM) minimization technique $f(A, B, C, D) = \sum m(0, 1, 3, 7, 8, 9, 11, 15)$	10	CO1
Q8	Design a sequential circuit to generate the sequence $0 \rightarrow 3 \rightarrow 1 \rightarrow 7 \rightarrow 5 \rightarrow 0$ using T flip-flops	10	CO2
Q9	a. Explain briefly about the applications of flipflops. b. Design a 4-bit Johnson (Twisted Ring) Counter with appropriate timing diagram.  OR  a. Explain briefly the operation of Parallel Input Serial Output Shift Register (PISO). b. Design a 4-bit Ring Counter with appropriate timing diagram.	10	CO2
<b>SECTION-C</b> <b>(2Qx20M=40 Marks)</b>			
Q10	a) Explain the various addressing modes of 8085 microprocessors with example. b) Describe briefly the bus structure of 8085 with a block diagram	10+10	CO4
Q11	a. Write the encoded digital signal by quantizing an analog signal of 10V (peak-to-peak) into 8-levels. b. Explain a 3-bit parallel-comparator (FLASH) A/D converter with a neat and clear diagram.  OR	5+15	CO3
	a. Convert the 8-bit digital value 10110101 to its equivalent analog value (Consider $K = \frac{R_f}{2^7 R} V_R = 1$ ). b. Explain a 3-bit weighted resistor D/A converter with a neat and clear diagram.	5+15	CO3