

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, April/May 2018

SET-1

Course: Analog Electronics-I (ECEG 2011)
Program: B.Tech ECE
Time: 03 hrs.

Semester: IV

Max. Marks: 100

SECTION A

S. No.		Marks	CO
Q 1	Define I_{CBO} and I_{CEO} . How are they different? How are they related? Are they typically close in magnitude?	4	CO1
Q 2	What will happen to the output AC signal if the DC level is insufficient? Sketch the effect on the waveform.	4	CO1
Q 3	Apply the proper biasing between drain and source and sketch the depletion region for $V_{GS} = 0$ V.	4	CO3
Q 4	What are the major differences between the collector characteristics of a BJT transistor and the drain characteristics of a JFET transistor? Compare the units of each axis and the controlling variable.	4	CO3
Q 5	What is the reactance of a 10- μ F capacitor at a frequency of 1 kHz? For networks in which the resistor levels are typically in the kilo-ohm range, is it a good assumption to use the short-circuit equivalence for the conditions just described? How about at 100 kHz?	4	CO2

SECTION B

Q 6	For the network of Fig. 1, $V_D = 9$ V. Determine: (a) I_D . (b) V_S and V_{DS} . (c) V_G and V_{GS} . (d) V_P .	10	CO2
-----	--	----	-----

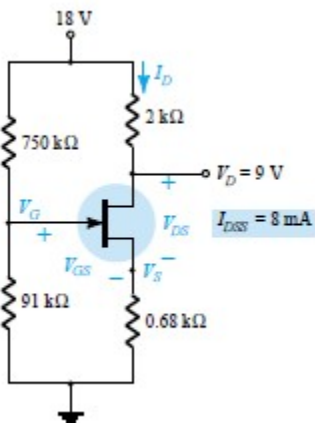


Fig 1

Q 7 For the network of Fig.2:
 (a) Determine Z_i and Z_o .
 (b) Find A_v and A_i .

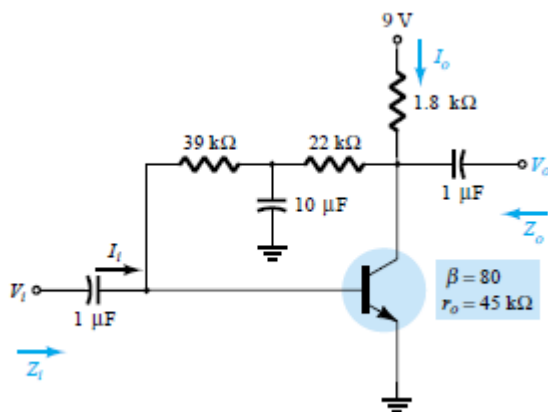


Fig.2

10 CO1

Q 8 Determine Z_i , Z_o , and A_v for the network of Fig. 3 if $y_{fs} = 3000 \mu S$ and $y_{os} = 50 \mu S$.

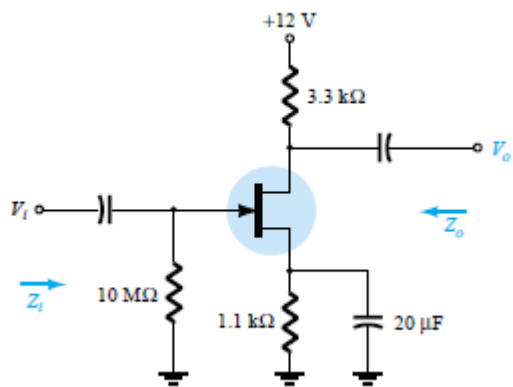


Fig. 3

10 CO5

Q 9 (a) What is the significant difference between the construction of an enhancement-


10 CO4

	<p>type MOSFET and a depletion-type MOSFET?</p> <p>(b) Sketch a p-channel enhancement-type MOSFET with the proper biasing applied ($V_{DS} > 0 V$, $V_{GS} = V_T$) and indicate the channel, the direction of electron flow, and the resulting depletion region.</p>		
SECTION-C			

Q 11

Given the typical values of $h_{ie} = 1 \text{ k}\Omega$, $h_{re} = 2 \times$

10^{-4} , and $A_v = -160$ for the input configuration of Fig. 4:

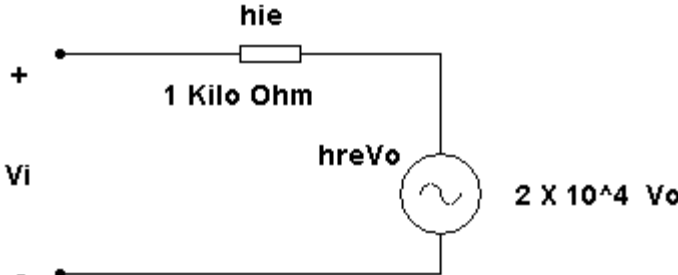	<p>(a) Determine V_o in terms of V_i.</p> <p>(b) Calculate I_b in terms of V_i.</p> <p>(c) Calculate I_b if $h_{re}V_o$ is ignored.</p> <p>(d) Determine the percent difference in I_b using the following equation:</p> $\% \text{ difference in } I_b = \frac{I_b(\text{without } h_{re}) - I_b(\text{with } h_{re})}{I_b(\text{without } h_{re})} \times 100\%$ <p>(e) Is it a valid approach to ignore the effects of $h_{re}V_o$ for the typical values employed in this example?</p> <div style="text-align: center;">  <p>The diagram shows a circuit with two terminals on the left. The top terminal is marked with a '+' sign and the bottom with a '-' sign. The voltage across these terminals is labeled V_i. A resistor labeled h_{ie} with a value of '1 Kilo Ohm' is connected between the top terminal and a central node. From this central node, a dependent current source labeled $h_{re}V_o$ with a value of $2 \times 10^4 V_o$ is connected to the bottom terminal. The current source is represented by a circle with a tilde symbol inside.</p> </div> <p>Fig.4</p>	20	CO3
<p>Q 12</p>	<p>For the self-bias JFET network of Fig.5:</p> <p>(a) Determine A_{vNL}, Z_i, and Z_o.</p> <p>(b) Sketch the two-port model with the parameters determined in part (a) in place.</p> <p>(c) Determine A_v and A_{vs}.</p> <p>(d) Change R_L to $6.8 \text{ k}\Omega$ and R_{sig} to $1 \text{ k}\Omega$ and calculate the new levels of A_v and A_{vs}. How are the voltage gains affected by changes in R_{sig} and R_L?</p> <p>(e) For the same changes as part (d), determine Z_i and Z_o. What was the impact on both impedances?</p>	20	CO5

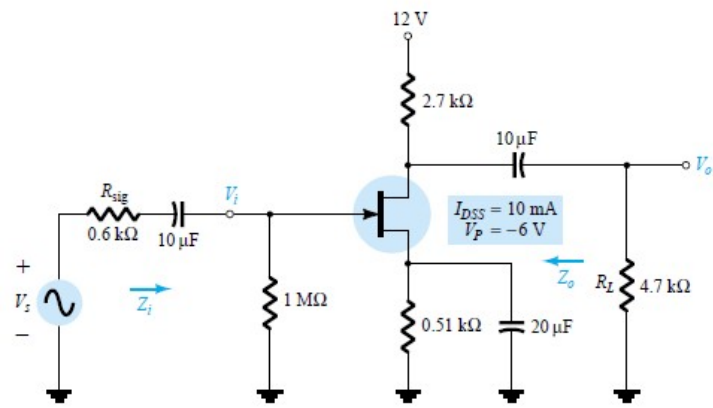


Fig.5

Name:	
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, April/May 2018


SET-2

Course: Analog Electronics -I (ECEG 2011)	Semester: IV
Program: B.Tech ECE	Max. Marks: 100
Time: 03 hrs.	

SECTION A

S. No.	Question	Marks	CO
Q 1	Can you think of the analogy that would explain the importance of the DC level on the resulting AC gain?	4	CO1
Q 2	In general, comment on the polarity of the various voltages and direction of the currents for an n-channel JFET versus a p-channel JFET.	4	CO2
Q 3	With the help of small signal transistor model define the phase relationship of input and output waveform. Define the above statement with the valid equations.	4	CO1
Q 4	Describe in your own words why I_G is effectively zero amperes for a JFET transistor.	4	CO5
Q 5	Why is the terminology field effect appropriate for this important three-terminal device FET?	4	CO4

SECTION B

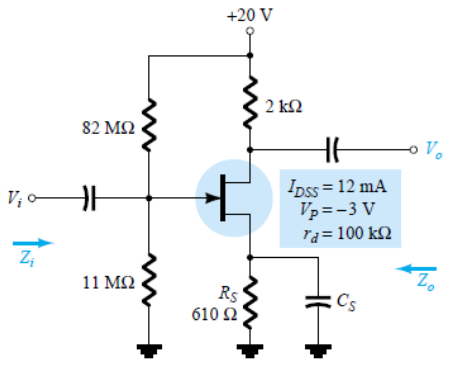Q 6	<p>Determine Z_i, Z_o, and V_o for the network of Fig. 1 if $V_i = 20$ mV.</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Fig 1</p>	10	CO2
Q 7	<p>For the common-base network of Fig. 2:</p> <p>(a) Determine Z_i and Z_o.</p> <p>(b) Calculate A_v and A_i.</p> <p>(c) Determine α, β, r_e, and r_o.</p>	10	CO4

$h_{fb} = -0.992$
 $h_{ib} = 9.45 \Omega$
 $h_{ob} = 1 \mu\text{A/V}$

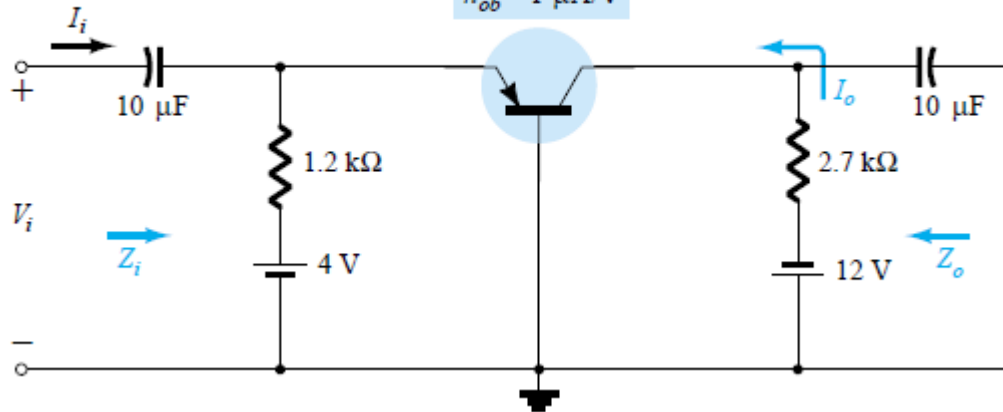


Fig.2

Q 8 Does the current of an enhancement-type MOSFET increase at about the same rate as a depletion-type MOSFET for the conduction region? Carefully review the general format of the equations, and if your mathematics background includes differential calculus, calculate dI_D/dV_{GS} and compare its magnitude.

10

CO5

Q 9 For the cascaded system of Fig. 3 with two identical stages, determine:

- The loaded voltage gain of each stage.
- The total gain of the system, A_v and A_{vs} .
- The loaded current gain of each stage.
- The total current gain of the system.
- How Z_i is affected by the second stage and R_L .
- How Z_o is affected by the first stage and R_s .
- The phase relationship between V_o and V_i .

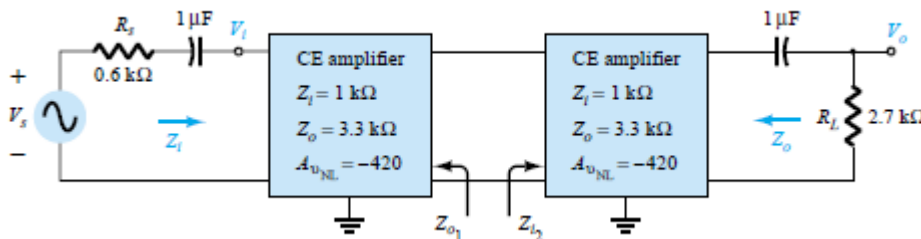


Fig. 3

10

CO4

Q 10 For the network of Fig. 4:

- Determine Z_i and Z_o .
- Find A_v and A_i .

10

CO1

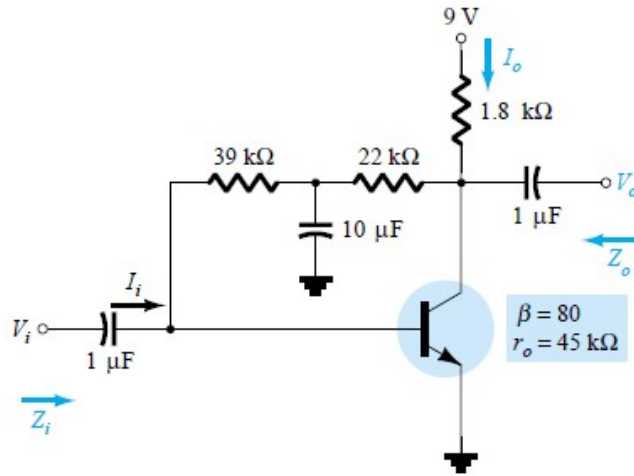


Fig. 4

Section C

Q 11

1. For the self-bias JFET network of Fig.5:

20

CO2

(a) Determine A_{vNL} , Z_i , and Z_o .

(b) Sketch the two-port model with the parameters determined in part (a) in place.

(c) Determine A_v and A_{vs} .

(d) Change R_L to $6.8 \text{ k}\Omega$ and R_{sig} to $1 \text{ k}\Omega$ and calculate the new levels of A_v and A_{vs} . How are the voltage gains affected by changes in R_{sig} and R_L ?

(e) For the same changes as part (d), determine Z_i and Z_o . What was the impact on both impedances?

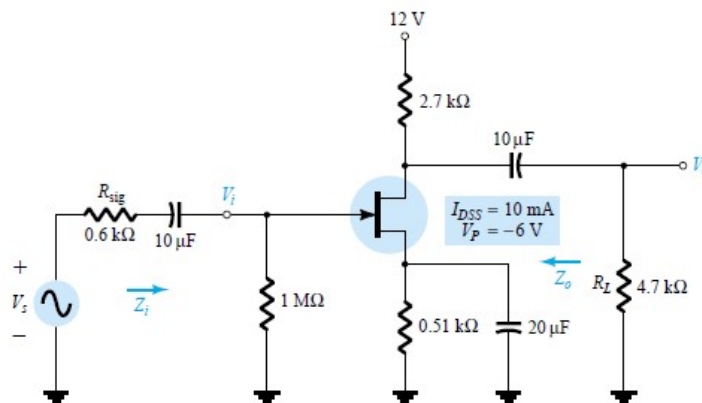


Fig.5

Q 12

For the source-follower network of Fig. 6:

- (a) Determine A_{vNL} , Z_i , and Z_o .
- (b) Determine A_v and A_{vs} .
- (c) Change R_L to $4.7\text{ k}\Omega$ and calculate A_v and A_{vs} . What was the effect of increasing levels of R_L on both voltage gains?
- (d) Change R_{sig} to $1\text{ k}\Omega$ (with R_L at $2.2\text{ k}\Omega$) and calculate A_v and A_{vs} . What was the effect of increasing levels of R_{sig} on both voltage gains?
- (e) Change R_L to $4.7\text{ k}\Omega$ and R_{sig} to $1\text{ k}\Omega$ and calculate Z_i and Z_o . What was the effect on both parameters?

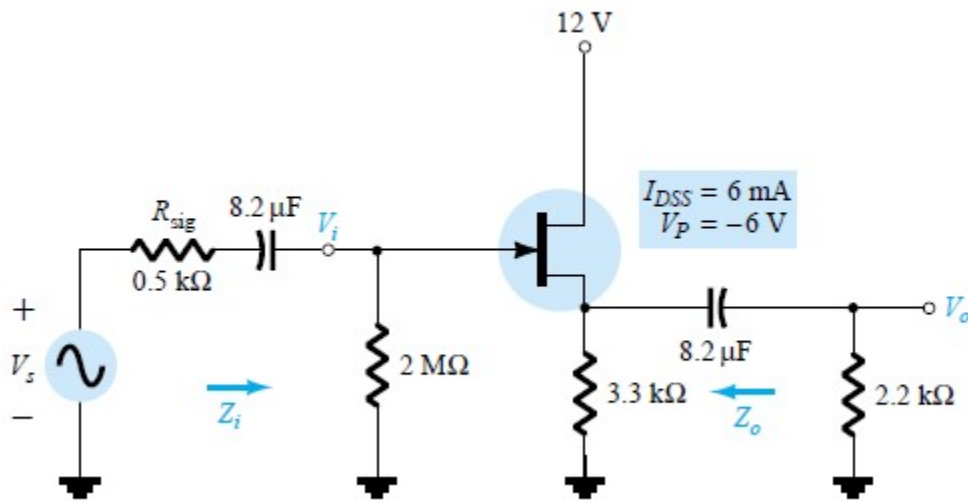


Fig.6

20

CO2