


QUESTION PAPER

| | |
|------------------------|---|
| Name: Enrolment No: |  |
|------------------------|---|


UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2018

Course: Analog and Digital Electronics (ECEG-2002)
Program: B. Tech- Mechatronics
Time: 03 hrs.

Semester: III
Max. Marks: 100

Instructions: Attempt all the sections.

SECTION A (20 Marks)
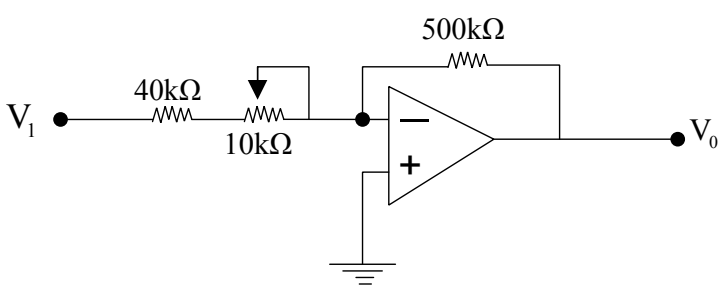
| S. No. | Answer all the questions. | Marks | CO |
|--------|---|-------|-----|
| Q 1 | Draw the circuit diagram of a single stage transistor amplifier, state the function of each component used in this circuit. | 4 | CO1 |
| Q 2 | The voltage gain of an amplifier without feedback is 1000. It decreases to 100 with feedback. Evaluate the feedback factor. | 4 | CO1 |
| Q 3 | Evaluate the range of the voltage gain adjustment in the circuit shown in Fig. (1) as, <div style="text-align: center; margin: 10px 0;">  </div> <p style="text-align: center;">Fig. (1)</p> | 4 | CO2 |
| Q 4 | Write the Boolean expression for the logic diagram given below and simplify it as much as possible. | 4 | CO3 |

 


Fig. (2)

Q 5 Sketch the block diagram of the combinational and sequential logic circuits. How both are differing on the basis of memory element and time dependent operation.

4

CO4

SECTION B (40 Marks)

Answer all the questions.

Q 6 Design a logic gate diagram of the obtained minimize expression using Universal 'NOR' gate.
The Boolean expression is:

10

CO3

$$Y = A + B \left(AC + \left(B + \bar{C} \right) D \right)$$

Q 7 Determine the output voltage of the circuit shown in Fig. (3).

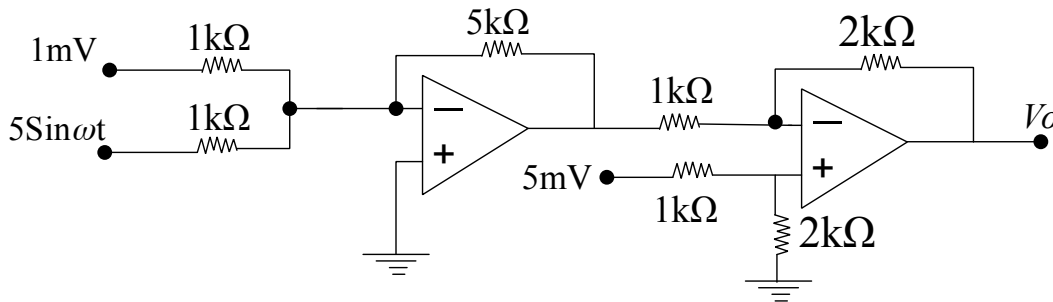


Fig.(3)

10

CO2

Q 8 Find the minimal sum of product for the Boolean expression $F = \sum m(1, 2, 3, 7, 8, 9, 10, 11, 14, 15)$ using Quine- McCluskey method.

10

CO3

Q 9 **Attempt both the parts:**

- (a) Elucidate the data transmission operation in the shift registers.
- (b) Design and analyze the operation of a 4-bit serial in- serial out shift register.

10

CO4

SECTION-C (40 Marks)

Answer all the questions.


Q 10 Design the combinational logic circuit for
(i) an Even Parity Bit Generator for a 4-bit (A, B, C, D) input data
(ii) an Odd Parity Bit Generator for a 4-bit (A, B, C, D) input data

10+10

CO3

| | | | |
|------|---|-------|-------------|
| Q 11 | <p>• Attempt both the parts:</p> <p>(a) Design a combinational logic circuit diagram that accepts a 4-bit Gray code (G4, G3, G2, G1) and provide 4-bit binary code (B4, B3, B2, B1).</p> <p>(b) Design and analyze the operation of a synchronous mode-6 Gray code converter using 'T' Flip-flop.</p> <p style="text-align: center;">OR</p> <p>Implement the following function using 8:1 MUX-</p> $F(x,y,z) = \sum m (0, 2, 3, 5)$ | 10+10 | CO3/ CO4 |
|------|---|-------|-------------|

QUESTION PAPER

| | |
|------------------------|---|
| Name: Enrolment No: |  |
|------------------------|---|

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2018


Course: Analog and Digital Electronics (ECEG-2002)
Program: B. Tech- Mechatronics
Time: 03 hrs.

Semester: III

Max. Marks: 100

Instructions: Attempt all the sections.

SECTION A (20 Marks)
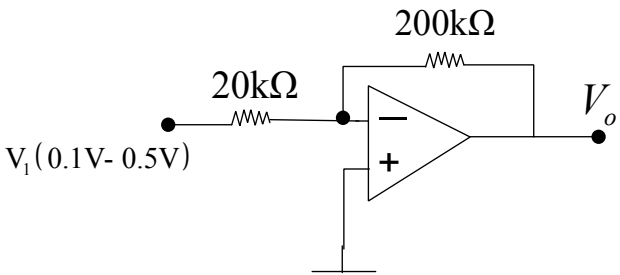
| S. No. | Answer all the questions. | Marks | CO |
|--------|--|-------|-----|
| Q 1 | Given $h_{ie} = 2.4k\Omega$, $h_{fe} = 100$, $h_{re} = 4 \times 10^{-4}$ and $h_{oe} = 25\mu S$. Sketch the common emitter hybrid equivalent model. | 4 | CO1 |
| Q 2 | A single stage transistor amplifier has a voltage gain of 600 without feedback and 50 with feedback. Find the percentage of output which is feedback to the input side. | 4 | CO2 |
| Q 3 | What is the range of the output voltage in the circuit of Fig. (1). If the input voltage can vary from 0.1V to 0.5V ? <div style="text-align: center; margin-top: 20px;">  <p>Fig. (1)</p> </div> | 4 | CO3 |

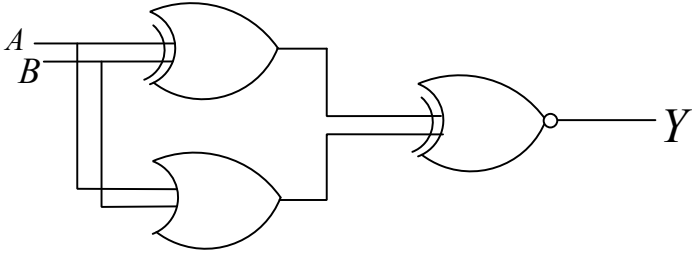
| | | | |
|-----|---|---|-----|
| Q 4 | Redraw the circuit given in Fig. (2) after simplification  | 4 | CO3 |
|-----|---|---|-----|

Fig. (2)

| | | | |
|-----|--|---|-----|
| Q 5 | Attempt all the parts: (i) $(158)_{BCD} \rightarrow (?)_2 \rightarrow (?)_{10}$ (ii) $(1246)_{10} \rightarrow (?)_{\text{Excess-3 code}}$ (iii) $(1011110)_2 \rightarrow (?)_{\text{Gray Code}}$ | 4 | CO4 |
|-----|--|---|-----|

SECTION B (40 Marks)

Answer all the questions.

| | | | |
|-----|--|----|-----|
| Q 6 | Minimize the minterm using (i) SOP and (ii) POS expressing using K-map $F(ABCD) = \sum m(2, 3, 6, 7, 10, 11, 12)$ | 10 | CO4 |
|-----|--|----|-----|

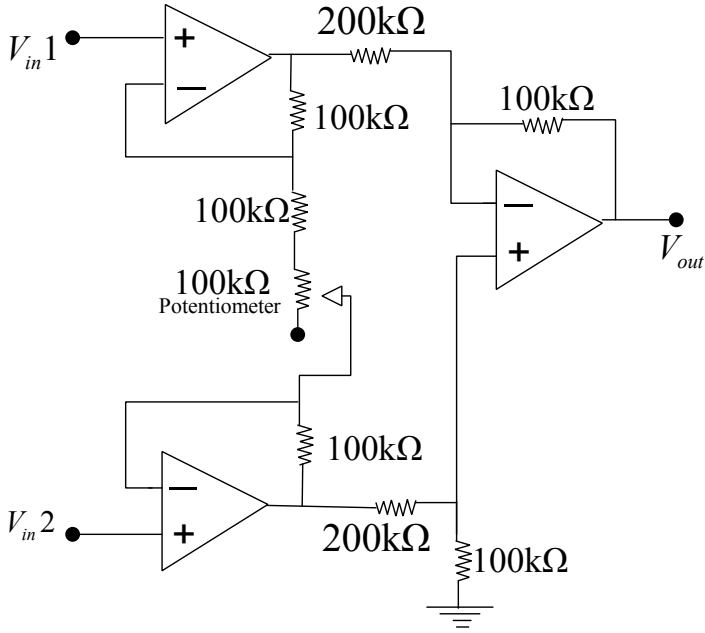
| | | | |
|-----|---|----|-----|
| Q 7 | The circuit shown in Fig. (3) is an instrumentation amplifier. Determine the range which its gain can be varied if potentiometer is varied over its entire range.  | 10 | CO2 |
|-----|---|----|-----|

Fig. (3)

| | | | |
|-----|---|----|-----|
| Q 8 | Draw the logic diagram using only two input NAND gates to implement the | 10 | CO3 |
|-----|---|----|-----|

| | | | |
|-----------------------------|--|--------------|---------------------|
| | <p>following Boolean expression</p> $F = (AB + \bar{A}\bar{B}) (C\bar{D} + \bar{C}D)$ | | |
| Q 9 | <p>Design and analyze the operation of parallel in- parallel out shift register.</p> <p style="text-align: center;">OR</p> <p>Design and analyze the operation of 3-bit up counter, which has counting sequence 000, 001, 010, 011, 100, 101, 110, 111, 000, Using J-K Flip-flops.</p> | 10 | CO4 |
| SECTION-C (40 Marks) | | | |
| | Answer all the questions. | | |
| Q 10 | <p>Design the logic diagram using NAND universal gate of obtained reduced expression of minimal expression for</p> $F = \sum m(6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$ <p>using Quine- McCluskey method.</p> | 20 | CO3 |
| Q 11 | <ul style="list-style-type: none"> • Attempt both the parts: (a) Design a synchronous BCD counter using J-K Flip-flops. (b) Design a circuit that can be built using AOI logic and outputs a '1' when a 4-bit hexa-decimal input is an odd number from 0 to 9. <p style="text-align: center;">OR</p> <p>Design a 5-bit comparator using a single 7485 4-bit comparator.</p> | 10+10 | CO4/ CO3 |