

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, December 2018

Programme Name: B Tech Mechatronics

Course Name : Network Theory

Course Code : ELEG204

Nos. of page(s) : 4

Semester : VII

Time : 03 hrs


Max. Marks : 100

Instructions:



- Attempt all questions as per the requirement.
- Assume any data if required and indicate the same clearly. Unless otherwise indicated symbols and notations have their usual meanings.
- Strike off all unused blank pages

SECTION A (20 Marks)

S.No.		Marks	CO
Q1	<p>Determine and at terminals 1-2 of circuit shown in Fig.1</p> <p style="text-align: center;">Fig.1</p>	4	CO1
Q2	<p>The Z-parameter matrix for two port network shown in fig. is $\begin{bmatrix} j2\omega & j\omega \\ j\omega & 3+j2\omega \end{bmatrix}$</p> <p>Where entries are in Ω, suppose $Z_b(j\omega) = R_b + j\omega$</p> <p>Determine the value of Z_a, R_b and Z_c</p>	4	CO2
Q3	<p>A 2-port network is represented by the following equations: $V_1 = 60 I_1 + 20 I_2$ $V_2 = 20 I_1 + 40 I_2$</p> <p>Calculate the ABCD parameters for this network.</p>	4	CO2

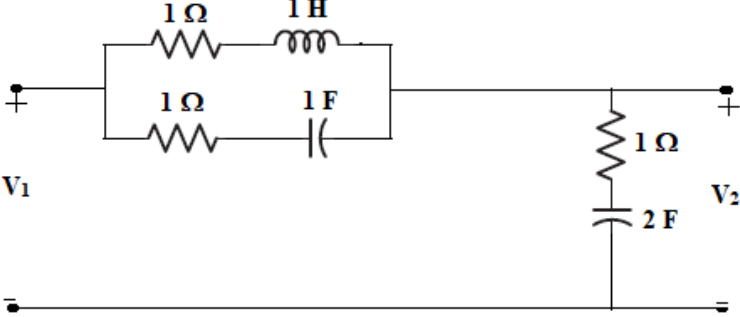Q4	Write properties of Hurwitz polynomial.	4	CO4
Q5	<p>Find the transfer function $H(s) = V_2(s)/V_1(s)$ for the given network shown in Fig.2</p>  <p style="text-align: center;">Fig.2</p>	4	CO4

SECTION B (40 Marks)

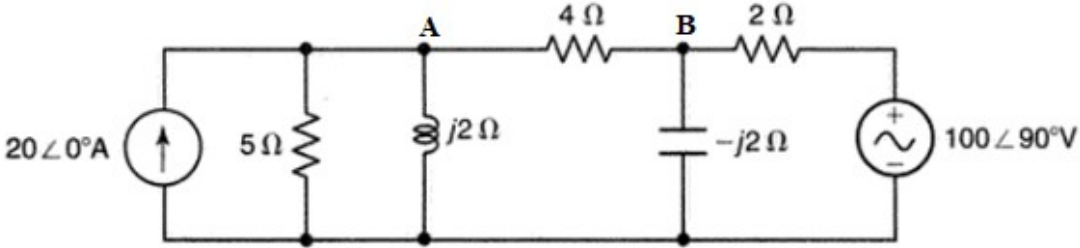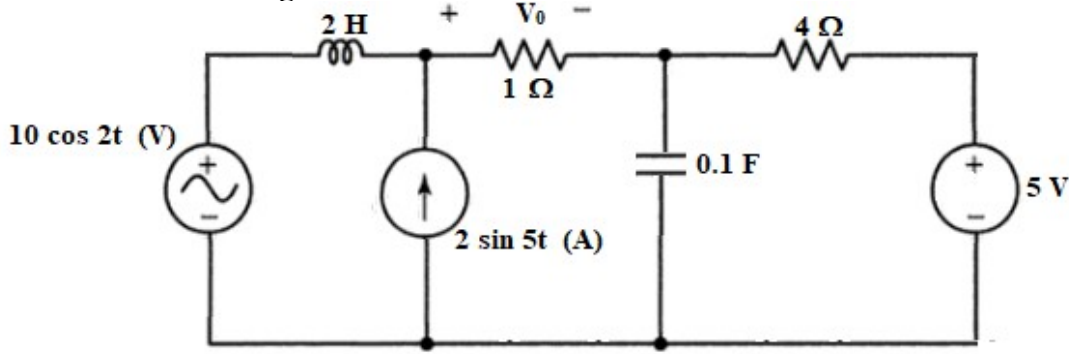Q6	<p>(a) In the circuit shown in Fig. 3, determine the steady state current in 4 Ω resistor using Thevenin's theorem.</p>  <p style="text-align: center;">Fig. 3</p> <p style="text-align: center;">Or</p> <p>(b) By using super position theorem determine the voltage V_0 across 1 Ω resistor in the circuit shown in Fig. 4</p>  <p style="text-align: center;">Fig. 4</p>	8	CO1
Q7	For the network shown in Fig.5 determine the z and y parameters	8	CO2

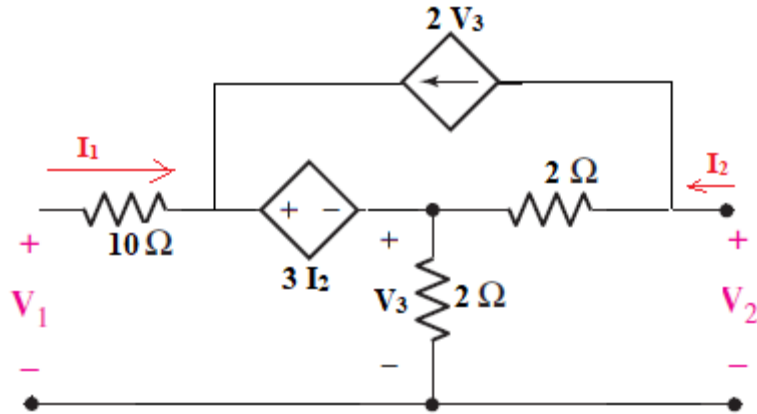


Fig.5
Or

The ABCD parameters of a two-port network shown in Fig.6 are $\begin{bmatrix} 4 & 20 \\ 0.1 & 2 \end{bmatrix}$. The output is connected to the variable load R_L for maximum power transfer. Calculate R_L and the maximum power transfer.

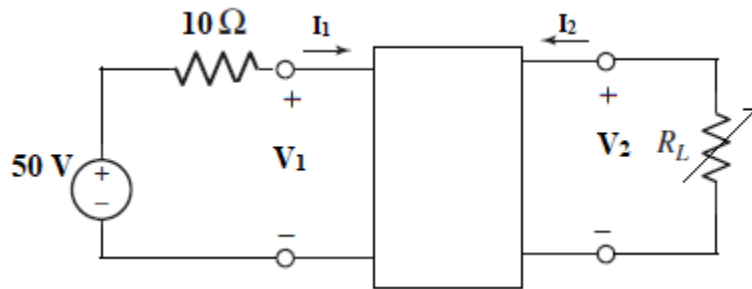


Fig.6

Q8 (a) Draw pole-zero plot for $V(s) = \frac{5s}{s^2 + 7s + 12}$. Determine the time domain expression $v(t)$ from its transform $V(s)$.

5+3

CO4

(b) Write the necessary conditions for network driving point impedance function.

Q9 Write incidence matrix and cut-set matrix of network shown in Fig.7

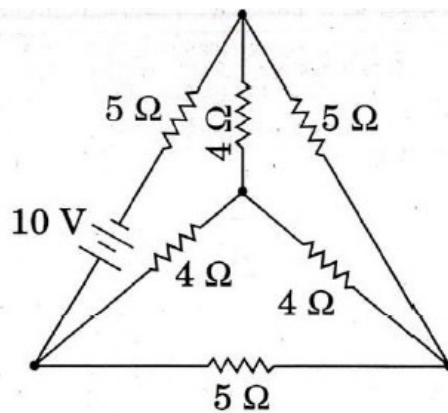




Fig.7

8

CO3

Q10	<p>(a) What is positive real functions? Write necessary and sufficient conditions for testing positive real functions.</p> <p>(b) Test whether the following polynomial are positive real or not.</p> $F(s) = \frac{10(s+1)^2}{(s+2)(s^2-6s+5)}$	5+3	CO4
-----	--	-----	-----

SECTION-C (40 Marks)

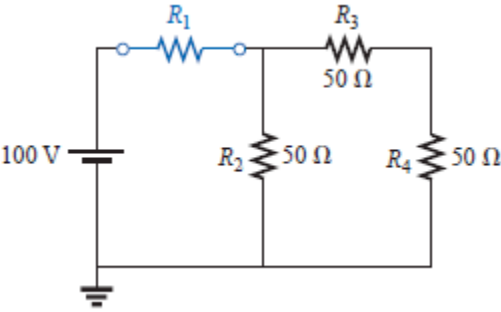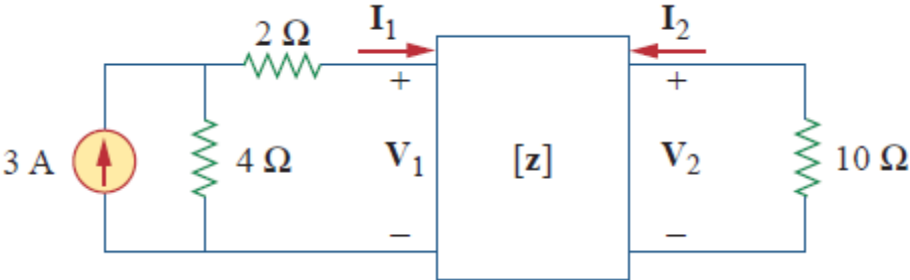Q11	<p>(a) Find the resistance R_1 of Fig.8 such that the resistor R_4 will receive maximum power.</p> <div style="text-align: center;">  <p>Fig.8</p> </div> <p>(b) For a two-port network shown in Fig.9 the z-parameters are $[Z] = \begin{bmatrix} 10 & -6 \\ -4 & 12 \end{bmatrix} \Omega$</p> <div style="text-align: center;">  <p>Fig.9</p> </div> <p>Calculate I_1, I_2, V_1 and V_2</p>	10+10	CO2
-----	---	-------	-----

Q12	<p>Synthesize the following impedance function in Foster-I and Foster- II forms of LC network:</p> $Z(s) = 8 \frac{(s^2+4)(s^2+25)}{s(s^2+16)}$ <p style="text-align: center;">Or</p> <p>A network function has poles at -2, -5 and zeros at 0, -4, -6. Taking the scaling factor to be 1, synthesize the function (i) as an impedance function in Foster's form and (ii) as an admittance function in Cauer form.</p>	20	CO4
-----	---	----	-----